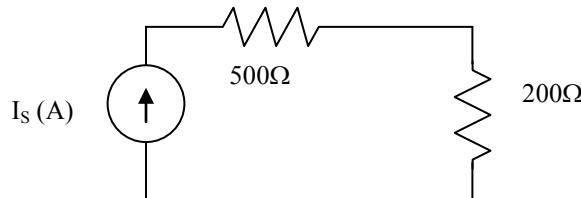


NAME: _____ SOLUTIONS _____

EEE 202: Test 1


2 Problems, Equal Credit, Closed-book/notes, one sheet of formulae allowed

Problem 1. In the following circuit, find “ I_s ” so that the power absorbed by the 200Ω resistance is $1W$.



$$P_{200} = I_s V_{200} = I_s^2 200 = 1 \Rightarrow I_s^2 = \frac{1}{200} \Rightarrow I_s = \frac{1}{10\sqrt{2}} = \frac{1}{14.14} = 0.07(A)$$

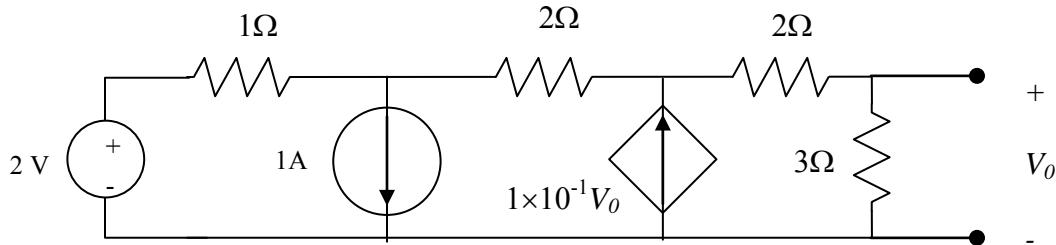Problem 2. Develop a set of equations to compute V_0 in the following circuit. Express your answers in matrix form.



Nodal analysis (4 nodes)

$$V_1 = 2$$

$$\begin{aligned} \frac{V_1 - V_2}{1} - 1 + \frac{V_3 - V_2}{2} &= 0 \\ \frac{V_2 - V_3}{2} + 0.1V_0 + \frac{V_4 - V_3}{2} &= 0 \Rightarrow \begin{bmatrix} 1 & 0 & 0 & 0 \\ 1 & -1.5 & 0.5 & 0 \\ 0 & 0.5 & -1 & 0.6 \\ 0 & 0 & 0.5 & -0.83 \end{bmatrix} V = \begin{bmatrix} 2 \\ 1 \\ 0 \\ 0 \end{bmatrix}, V_0 = V_4 \\ \frac{V_3 - V_4}{2} + \frac{0 - V_4}{3} &= 0 \\ V_0 &= V_4 \end{aligned}$$

Loop analysis (3 loops)


$$\begin{aligned} I_1 - I_2 &= 1 \\ I_2 - I_3 &= -0.1V_0 \\ -2 + I_1 1 + I_2 2 + I_3 (2+3) &= 0 \Rightarrow \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -0.7 \\ 1 & 2 & 5 \end{bmatrix} V = \begin{bmatrix} 1 \\ 0 \\ 2 \end{bmatrix}, V_0 = I_3 3 \\ V_0 &= I_3 3 \end{aligned}$$

Both result in the same solution: $V_0 = 0.423$.


Problem 1.

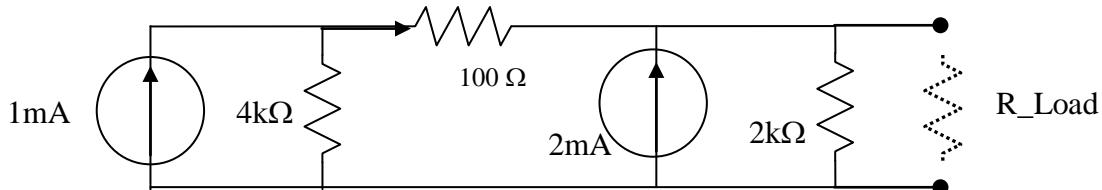Problem 1. Determine the Thevenin and Norton Equivalents for the circuit below (without the load).


$$V_{oc} = 4V \quad I_{sc} = 2.98mA \quad R_{TH} = 1.34k\Omega$$



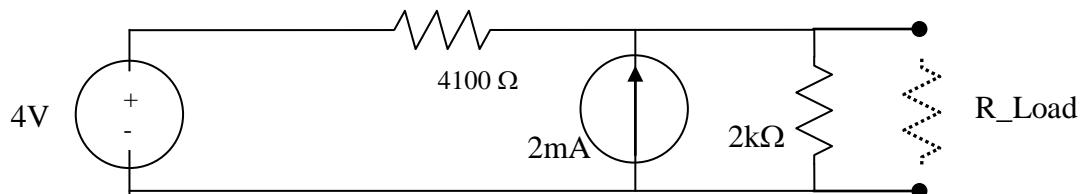Simplify with a source transformation: $I_s = 1mA$, $R = 4k \Rightarrow V_s = 4V$




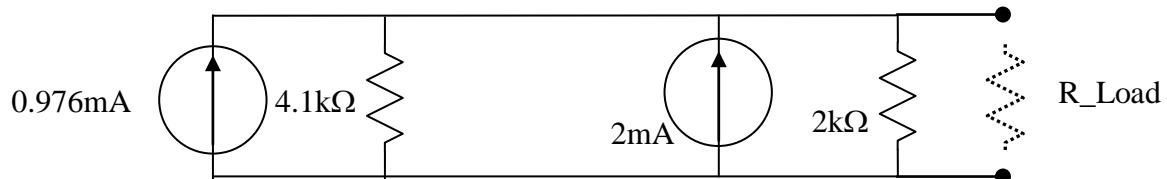Apply a second source transformation to obtain a single node pair circuit



It now follows easily that $I_{sc} = 2.98mA$, $R_{TH} = 4.1k||2k = 1.344k\Omega$, $V_{oc} = R_{TH}I_{sc} = 4V$

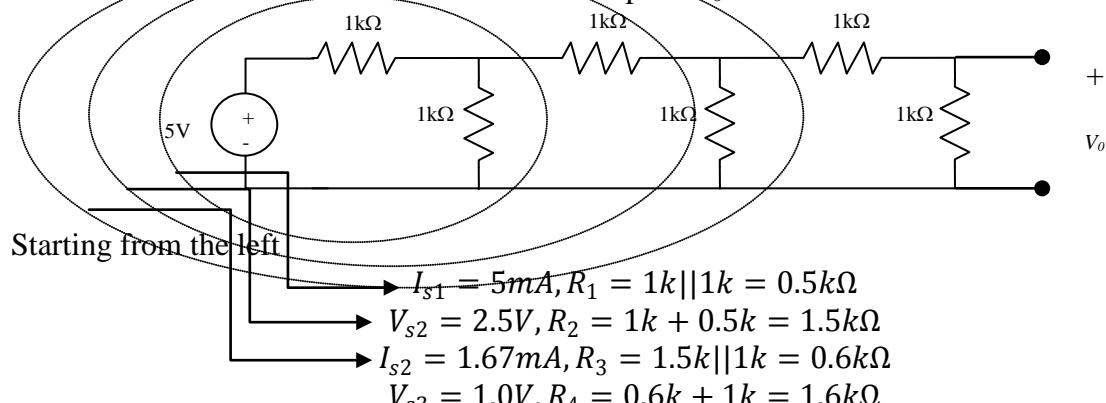Problem 2. Use Source Transformation to compute V_o for the circuit:



Finally, a voltage division yields

$$V_o = V_{s3} \frac{1k}{1.6k + 1k} = 0.385V$$

EEE 202: TEST 3

NAME: _____ SOLUTIONS _____

2 Problems, equal credit, 50', Closed Book&Notes, 1 sheet of formulae allowed

Problem 1.



The current across a 0.1nF capacitor is shown in the following figure. Plot the capacitor voltage. (Carefully label your plot.)

$$V = V(0) + \frac{1}{C} \int_0^t i(\tau) d\tau \Rightarrow$$

$$\text{At } t = 5, V(5) = V(0) + \frac{1}{1e-10} 20m \times 4m$$


$$\text{At } t = 7, V(7) = V(5) + \frac{1}{1e-10} (-20)m \times 2m$$

$V(0)$ is not given and it is an offset for the entire response.

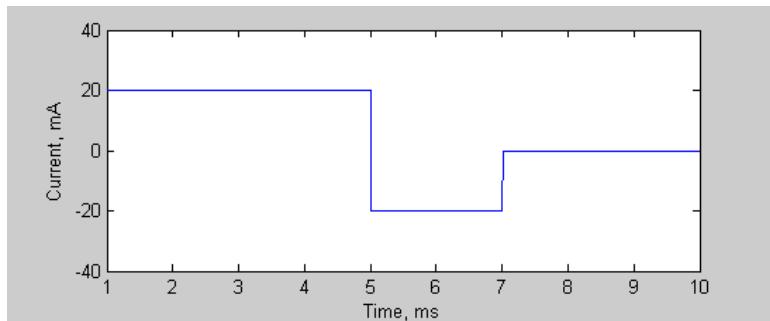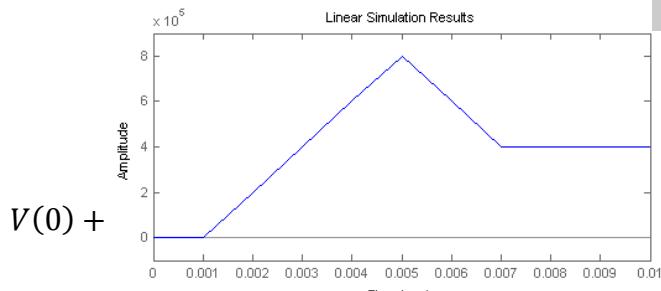

Problem 2. In the following circuit, find:

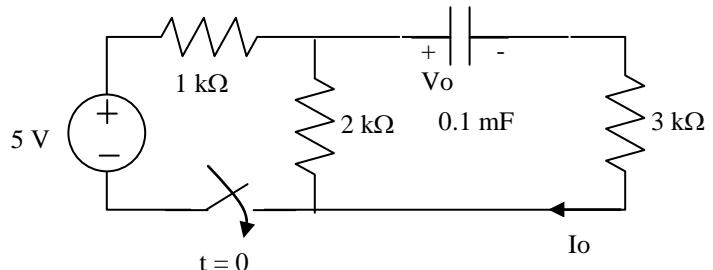1. The voltage V_o for $t > 0$.
2. The current I_o for $t > 0$.



$$t < 0: V_c(0^-) = 0 = V_c(0^+) = V_o(0^+)$$

$$t > 0: V_o(\infty) = 5 \times \frac{2}{1+2} = 3.33(V)$$

$$t > 0: R_{TH} = 3k + 2k||1k = \frac{11}{3}k(\Omega) \Rightarrow \tau = R_{TH} C = \frac{11}{3}k \times 0.1\text{m} = \frac{11}{30} = 0.367(\text{s})$$

$$t > 0: V(t) = V_o(\infty) + [V_o(0^+) - V_o(\infty)]e^{-t/\tau} = 3.33 - 3.33e^{-\frac{t}{0.367}}$$

$$t > 0: I_o(0^+) = 5m \frac{\frac{1}{3k}}{\frac{1}{1k} + \frac{1}{2k} + \frac{1}{3k}} = \frac{10}{11}m(A) \text{ (After using a source transformation and current division to find the current through the } 3\text{k resistance.)}$$

$$t > 0: I_o(\infty) = 0(A)$$

$$t > 0: R_{TH} = 3k + 2k||1k = \frac{11}{3}k(\Omega) \Rightarrow \tau = R_{TH} C = \frac{11}{3}k \times 0.1\text{m} = \frac{11}{30} = 0.367(\text{s})$$


$$t > 0: V(t) = I_o(\infty) + [I_o(0^+) - I_o(\infty)]e^{-t/\tau} = \frac{10}{11}e^{-\frac{t}{0.367}}$$

Note: We could get the same answer by observing that I_o is the current through the capacitor and using the formula $I_o = C \frac{dV_o}{dt}$.

EEE 202, TEST 4
NAME: _____ **SOLUTIONS**
Closed-book/notes, 3 problems, equal credit, 1 sheet of formulae allowed

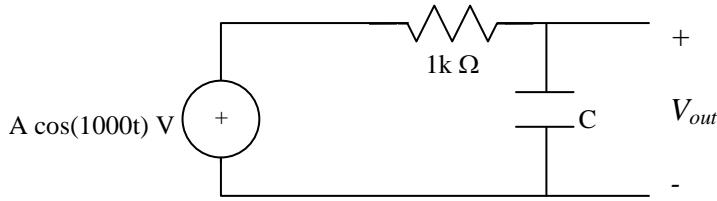Problem 1: RC-filters are often used to reduce the effect of high-frequency noise in circuits. In the following example, the voltage source represents a high frequency signal that is to be attenuated at the output (V_{out}).


Write an expression for V_{out} and determine the value of the capacitance C so that the amplitude of V_{out} is 100 times smaller than the amplitude of the source.



$$1. V_{out} = \frac{\frac{1}{jwC}}{R + \frac{1}{jwC}} V_{in} = \frac{1}{RCjw + 1} A\angle 0 = \frac{A}{\sqrt{R^2 C^2 w^2 + 1}} \angle -\tan^{-1}\left(\frac{RCw}{1}\right)$$

$$2. |V_{out}| = \frac{A}{\sqrt{R^2 C^2 w^2 + 1}} < \frac{A}{100} \Rightarrow R^2 C^2 w^2 + 1 > 100^2 \Rightarrow C \simeq \frac{100}{Rw} \Rightarrow C \simeq 100 \mu F$$

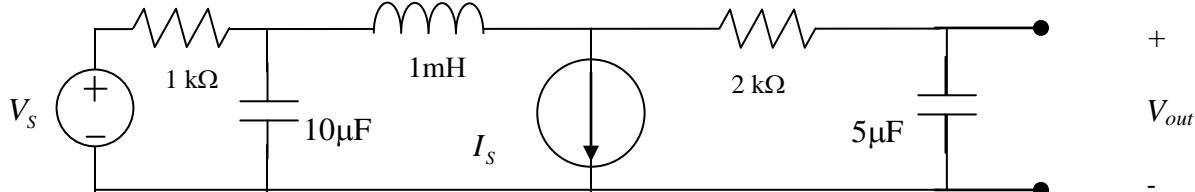Problem 2. In the following circuit, $I_S(t) = 0.001\cos(10t)$ (A), $V_S(t) = 2\cos(10t)$ (V). Write a set of equations to compute the voltage V_{out} . Express in a matrix form.



$$I_s = 0.001\angle 0, V_s = 2\angle 0^\circ, Z_L = j(10)(0.001) = j0.01, Z_{C1} = -j10k, Z_{C2} = -j20k$$

Loop analysis:


$$\begin{aligned} -2\angle 0 + I_1 1k + (I_1 - I_2)(-j10k) &= 0 \\ I_2 - I_3 &= 0.001\angle 0 \\ -2\angle 0 + I_1 1k + I_2 (j0.01) + I_3 (2k - j20k) &= 0 \\ V_{out} &= I_3 (-j20k) \end{aligned} \quad \text{or} \quad \begin{bmatrix} 1k - j10k & j10k & 0 \\ 0 & 1 & -1 \\ 1k & j0.01 & 2k - j20k \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 2 \\ 1m \\ 2 \end{bmatrix}$$

Nodal analysis: Simplify substituting V_s directly for the first node voltage

$$\begin{bmatrix} \frac{2-V_2}{1k} + \frac{-V_2}{-j10k} + \frac{V_3-V_2}{j10m} = 0 \\ \frac{V_2-V_3}{j10m} - 1m + \frac{V_4-V_3}{2k} = 0 \\ \frac{V_3-V_4}{2k} + \frac{-V_4}{-j20k} = 0 \end{bmatrix} \quad \text{or} \quad \begin{bmatrix} \frac{-1}{1k} + \frac{1}{j10k} + \frac{-1}{j10m} & \frac{1}{j10m} & 0 \\ \frac{1}{j10m} & \frac{-1}{j10m} + \frac{1}{2k} & \frac{1}{2k} \\ 0 & \frac{1}{2k} & \frac{-1}{2k} + \frac{1}{j20k} \end{bmatrix} V = \begin{bmatrix} -\frac{2}{1k} \\ 1m \\ 0 \end{bmatrix}, V_{out} = V_4$$

Closed-book/notes, 2 problems, equal credit, 1 sheet of formulae allowed

Problem 1: For the following circuit

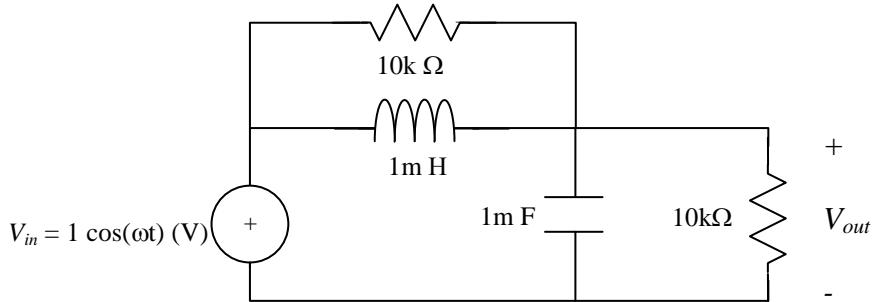

Find:

$$\text{The transfer function } \frac{V_{out}}{V_{in}} = \frac{\left(sC + \frac{1}{R}\right)^{-1}}{\left(\left(\frac{1}{sL} + \frac{1}{R}\right)^{-1} + \left(sC + \frac{1}{R}\right)^{-1}\right)} = \frac{R(Ls + R)}{R(Ls + R) + Rls(RCs + 1)} = \frac{\left(\frac{L}{R}s + 1\right)}{LCs^2 + \frac{2L}{R}s + 1}$$

- The resonant frequency $\omega_0 = \frac{1}{\sqrt{LC}} = 1e3 \text{ (rad/s)}$
- The damping ratio $\zeta = \frac{(2L)}{LC} \frac{1}{2\omega_0} = \frac{1}{R} \sqrt{\frac{L}{C}} = 0.1e - 3$

Problem 2: Sketch the Bode plot (magnitude and phase) for the transfer function

$$H(s) = \frac{1000(s + 1)}{(s + 10)^3}$$

