
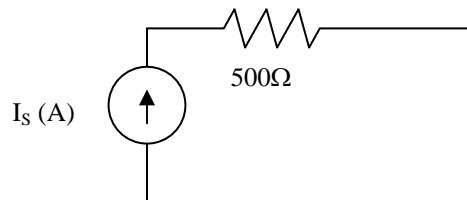


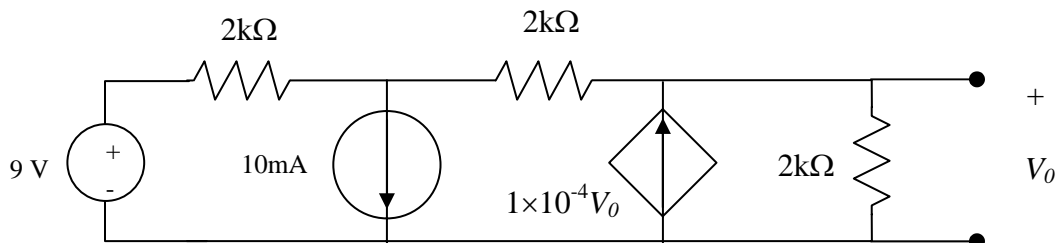Problem 1. In the following circuit, the unknown current source provides 1W of power. Find the value of the source current “ I_s .”



$$P = I_s V_s, \quad V_s = R I_s \Rightarrow P = R I_s^2 \Rightarrow I_s = \sqrt{\frac{1}{500}} = 0.045(A)$$

Problem 2. Develop a set of equations to compute V_o in the following circuit. Express your answers in matrix form.



Nodal Analysis

After writing the nodal equations, we obtain the following matrix form


$$\begin{bmatrix} 1 & 0 & 0 \\ \frac{1}{2k} & -\frac{1}{2k} - \frac{1}{2k} & \frac{1}{2k} \\ 0 & \frac{1}{2k} & -\frac{1}{2k} - \frac{1}{2k} + 1e-4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 9 \\ 0.01 \\ 0 \end{bmatrix}, V_o = V_3 = -4.23$$

Loop Analysis

After writing the loop equations (one super-mesh), we obtain the following matrix form

$$\begin{bmatrix} 2k & 2k & 2k \\ 1 & -1 & 0 \\ 0 & -1 & 1 - (1e-4)(2k) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 9 \\ 0.01 \\ 0 \end{bmatrix}, V_o = 2kI_3 = -4.23$$

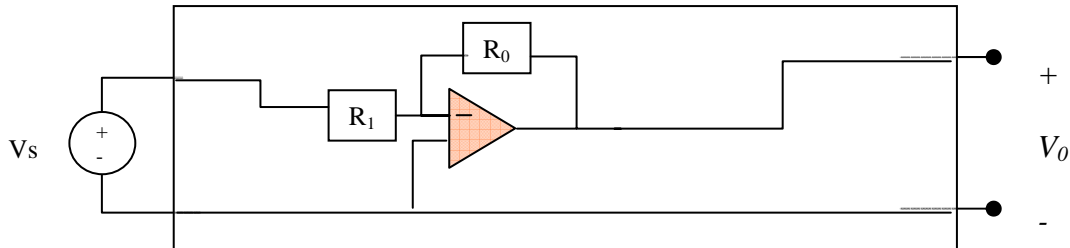
Problem 1. The following op-amp amplifier with $R_1 = 1\text{k}\Omega$ and $R_0 = 50\text{k}\Omega$ is used to amplify a sensor voltage V_s in the range $[0-1]\text{mV}$. Find the output voltage V_0 and the maximum current drawn from the sensor, when $V_s = 0.7\text{mV}$.



$$V_0 = -\frac{R_0}{R_1} V_s = -(50)(0.7)\text{mV} = -35\text{mV}$$

$$i_s = \frac{(V_s - 0)}{R_1} = \frac{0.7\text{m}}{1\text{k}} = 0.7\mu\text{A}$$

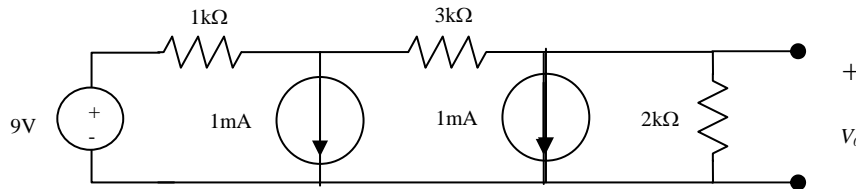Problem 2. Find the Thevenin equivalent of the following circuit:




Approach 1: Apply Nodal analysis to find I_{sc} , shorting the $2\text{k}\Omega$ resistance. This is easier because the short reduces the number of nodes. There are 2 nodes, $V_1=9\text{V}$ and V_2 . We have

$$\frac{V_2 - 9}{1\text{k}} + \frac{V_2}{3\text{k}} + 1\text{m} = 0 \Rightarrow V_2 = 6$$

To compute I_{sc} observe that the current out of the 3k resistor is $V_2/3\text{k} = 1\text{m} + I_{sc}$, hence, $I_{sc} = 1\text{mA}$. Next, the Thevenin resistance of the circuit is $(1\text{k}+3\text{k})\parallel 2\text{k} = (4/3)\text{k}\Omega$. Hence, $V_{oc} = (4/3)\text{V}$.

Approach 2: Apply successive source transformations to reduce the circuit starting from the left:

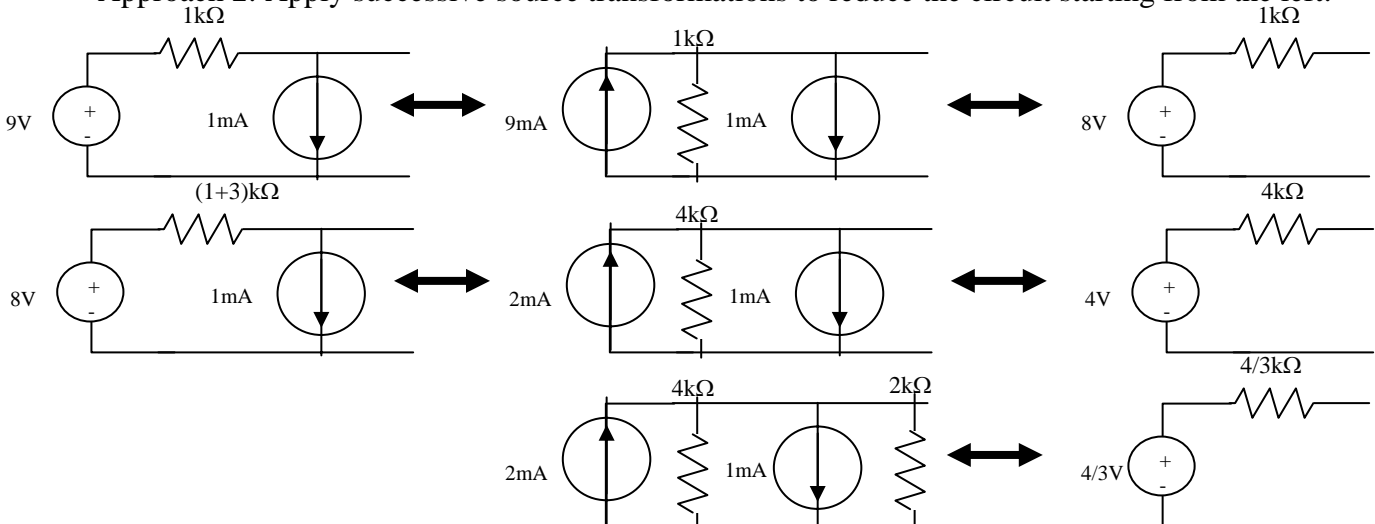

EEE 202: TEST 3

NAME: _____ SOLUTIONS _____


3 Problems, equal credit, 50', Closed Book&Notes, 1 sheet of formulae allowed

Problem 1.

1. A circuit voltage is described by $3\frac{dv}{dt} + 2v = 4\sin(t)$; $v(0)=1$. Find its time constant.

$$T = \frac{3}{2} = 1.5(\text{s})$$

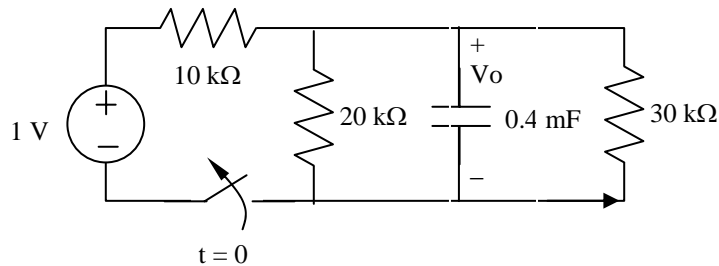
Problem 2. In the following circuit, find the voltage V_o for $t > 0$.



V_o is a continuous variable.

- $t < 0$, From voltage division: $V_o(0) = \frac{20k||30k}{10k+(20k||30k)} V_s = \frac{12k}{10k+12k} 1 = \frac{6}{11} = 0.55(V)$
- $t > 0$, $V_o(\infty) = 0(V)$
- $t > 0$, $R_{TH} = 20k||30k = 12k(\Omega) \Rightarrow T = R_{TH}C = 0.4m \times 12k = 4.8(s)$
- $t > 0$, $V_o(t) = FV + (IC - FV)e^{-\frac{t}{R_{TH}C}} = 0.55e^{-\frac{t}{4.8}}(V)$

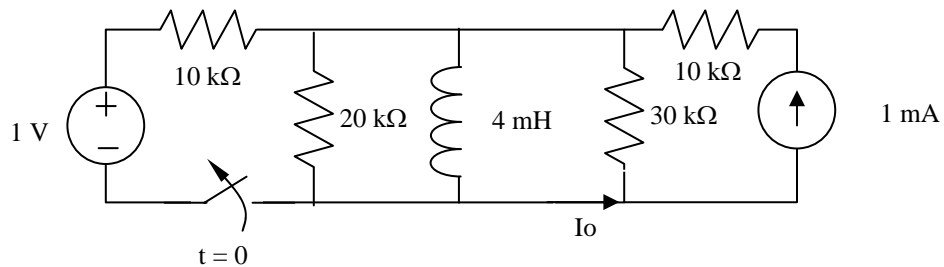Problem 3. In the following circuit, find the current I_o for $t > 0$.



I_o is a possibly discontinuous variable.


- $t < 0$, Perform a source transformation of the voltage source ($I_s = 0.1mA$, $R_s = 10k||20k = 6.7k$). Then, at steady-state, the inductor current is the sum of the two current sources $I_L(0) = 0.1m + 1m = 1.1m(A)$
- $t > 0$, Replace inductor with a current source to find I_C for I_o : 3 loops with currents I_1, I_2, I_3 (clock-wise, left-to-right), and loop equations $I_1 - I_2 = 1.1m, I_3 = -1m, 6.7kI_1 + 30k(I_2 - I_3) = 0$, from which, $I_o(0) = -I_2 = \frac{37.3}{36.7}m = 1.02m(A)$.
- $t > 0$, Replace inductor with a short: $I_o(\infty) = 1m(A)$, (i.e., all the current from the source).
- $t > 0$, $R_{TH} = 20k||30k = 12k(\Omega) \Rightarrow T = \frac{L}{R_{TH}} = \frac{1}{3}\mu(s)$
- $t > 0$, $I_o(t) = 1m + 20\mu e^{-3Mt}(A)$ (where, $M = 1e6$).

EEE 202, TEST 4

NAME: _____ SOLUTIONS _____

Closed-book/notes, 3 problems, equal credit, 1 sheet of formulae allowed

For the following circuit:

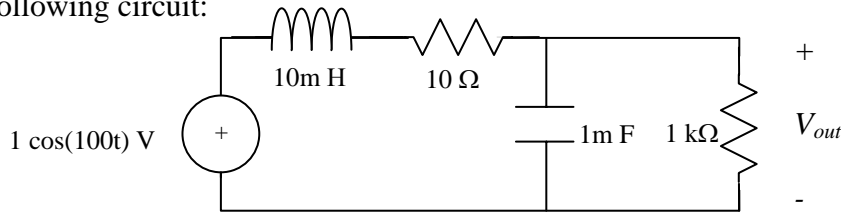

Problem 1: Find the steady-state voltage at the 1000 Ohm resistor (V_{out}).

At 100rad/s: $10mH \Rightarrow j$, $1mF \Rightarrow -10j$, $1mF || 1k \Rightarrow 0.1 - 10j$


Voltage division: $V_{out} = 1 \angle 0 \frac{0.1 - 10j}{j + 10 + 0.1 - 10j} = 0.50 - 0.55j = 0.74 \angle -48^\circ$

Problem 2: Find the average power dissipated by the 1000 Ohm resistor.

Current: $I_R = \frac{V_{out}}{1k} = 0.74m \angle -48^\circ$

Power: $P_{av} = \frac{1}{2} \frac{|V_{out}| |I_R|}{1k} \cos(\theta_v - \theta_i) = \frac{1}{2} 0.74^2 m = 0.27m(W)$

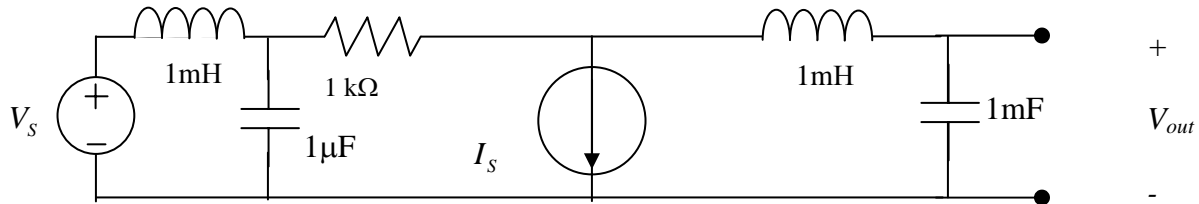Problem 3. In the following circuit, $I_S(t) = 0.001 \cos(100t)$ (A), $V_S(t) = 2 \cos(100t + 30^\circ)$ (V). Write a set of equations to compute the voltage V_{out} . Express in a matrix form.



$I_S = 0.001 \angle 0$, $V_S = 2 \angle 30^\circ$, $Z_L = j(100)(0.001) = j0.1$, $Z_{C1} = -j10k$, $R_{C2} = -j10$

Loop analysis:

$-2 \angle 30 + I_1 j0.1 + (I_1 - I_2)(-j10k) = 0$

$I_2 - I_3 = 0.001 \angle 0$ or

$(I_2 - I_1)(-j10k) + I_2(1k) + I_3(j0.1 - j10) = 0$

$V_{out} = I_4(-j10)$

$$\begin{bmatrix} -j(10k - 0.1) & j10k & 0 \\ 0 & 1 & -1 \\ j10k & 1k - j10k & -j9.9 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -2e^{j\frac{\pi}{6}} \\ 1m \\ 0 \end{bmatrix} = \begin{bmatrix} -1.73 - j1.00 \\ 0.001 \\ 0 \end{bmatrix}$$


Computing in MATLAB, $V_{out} = (-10.2 + j27.2)m = 29.1m \angle 110.7^\circ (V)$

EEE 202, TEST 5

NAME: _____ **SOLUTIONS** _____

Closed-book/notes, 2 problems, equal credit, 1 sheet of formulae allowed

Problem 1: For the following circuit

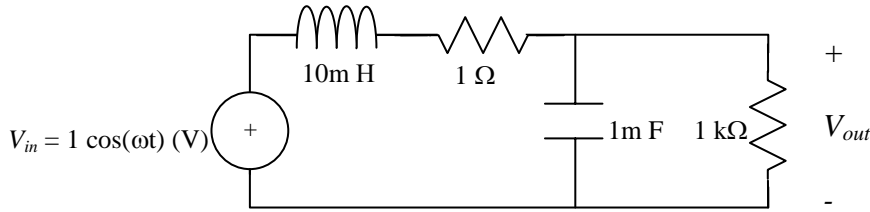

Find:


$$\text{The transfer function } \frac{V_{out}}{V_{in}} = \frac{(sC + \frac{1}{R_2})^{-1}}{sL + R_1 + (sC + \frac{1}{R_2})^{-1}} = \frac{1}{(sL + R_1)(sC + \frac{1}{R_2}) + 1} = \frac{1}{s^2LC + s(R_1C + \frac{L}{R_2}) + 1 + \frac{R_1}{R_2}} =$$

$$\frac{1/LC}{s^2 + s(\frac{R_1}{L} + \frac{1}{R_2C}) + \frac{1}{LC}(1 + \frac{R_1}{R_2})} = \frac{1/10\mu}{s^2 + s(\frac{1}{10m} + \frac{1}{1k1m}) + \frac{1}{10m1m}(1 + \frac{1}{1k})} = \frac{100,000}{s^2 + s(101) + 100,100} = \frac{100,000}{s^2 + s101 + (316.4)^2}$$

- The resonant frequency $\omega_0 = 316.4(\text{rad/s})$
- The damping ratio $\zeta = \frac{101}{(2)(316.4)} = 0.16$
- The quality factor $Q = \frac{1}{2\zeta} = 3.13$

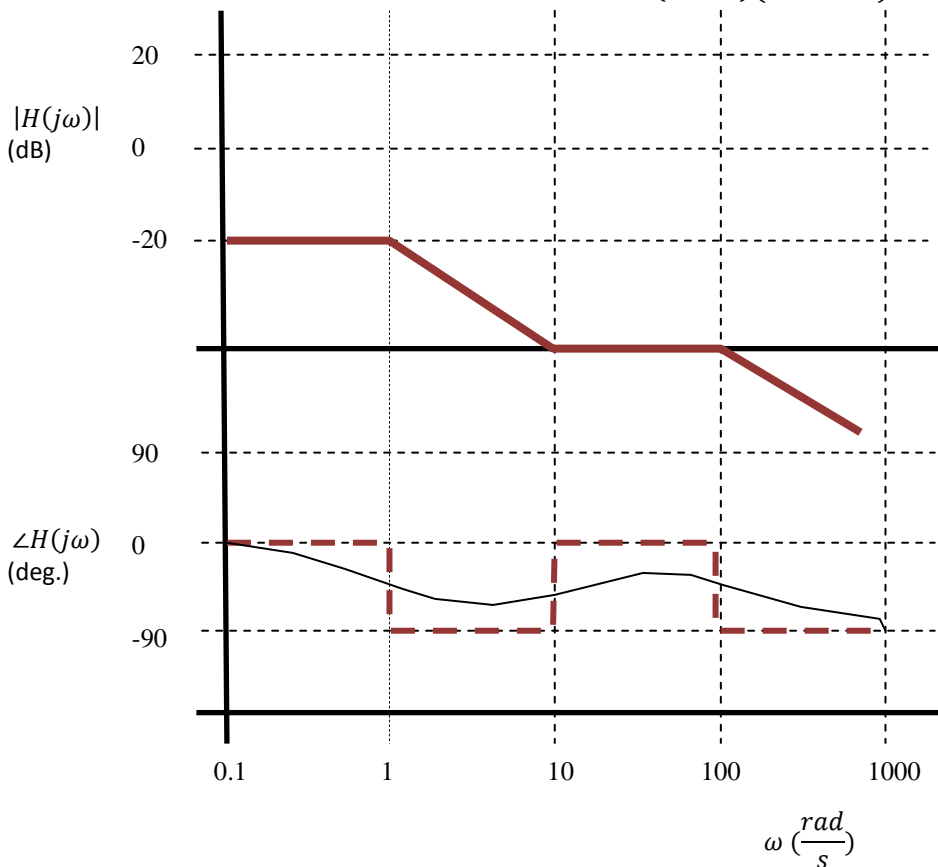Problem 2: Sketch the Bode plot (magnitude and phase) for the transfer function

$$H(s) = \frac{s + 10}{(s + 1)(s + 100)}$$



Corner Frequencies
Zeros: 10
Poles: 1, 100
DC-gain: 1/10 = -20dB

3.8 Find I_o in the network in Fig. P3.8 using nodal analysis.

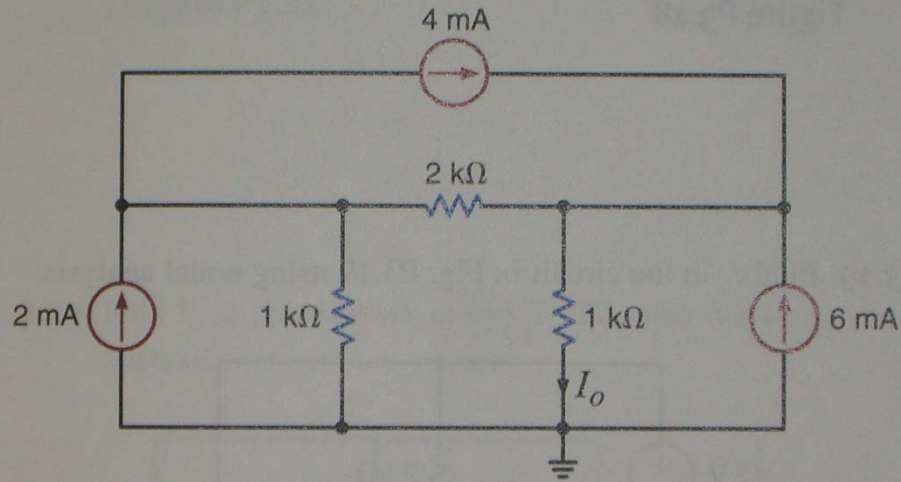


Figure P3.8

3.36 Find V_o in the network in Fig. P3.36 using nodal analysis.

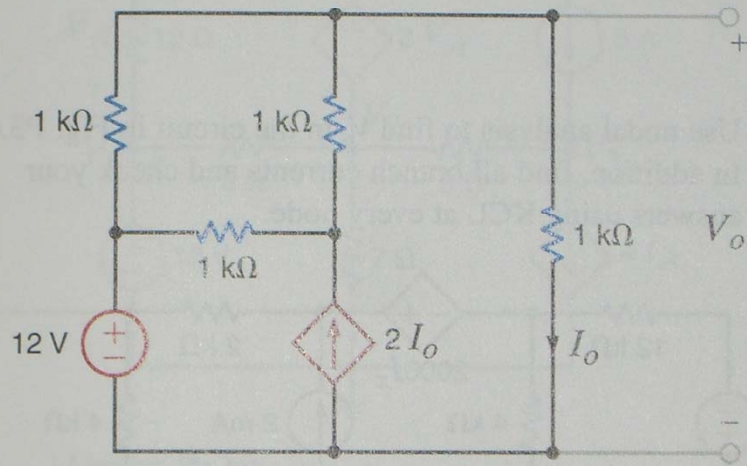


Figure P3.36

3.65 Find V_o in the network in Fig. P3.65 using loop analysis.

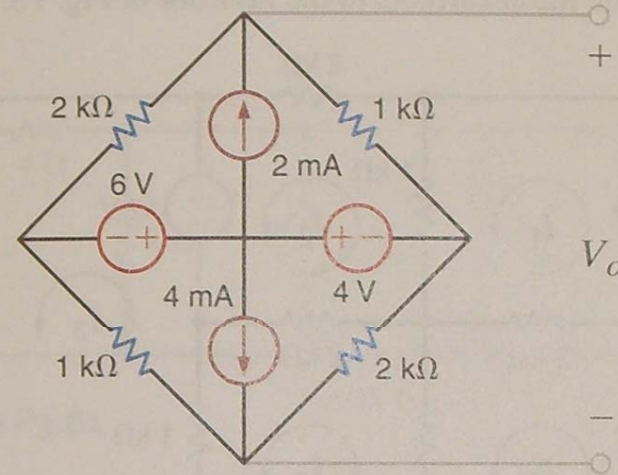


Figure P3.65

3.66 Find V_o in the circuit in Fig. P3.66 using loop analysis.


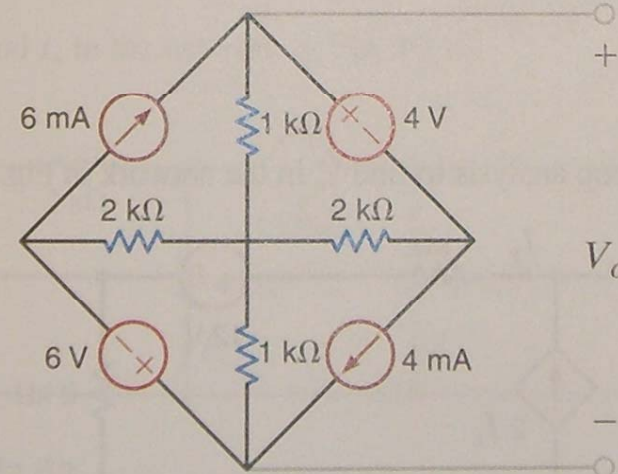


Figure P3.66

EEE202 HW 1.2 SOLUTIONS

3.8

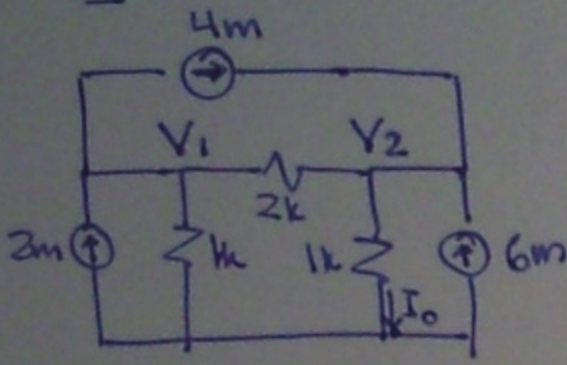

$$2m - 4m - \frac{V_1}{1k} + \frac{V_2 - V_1}{2k} = 0$$

$$\frac{V_1 - V_2}{2k} - \frac{V_2}{1k} + 6m + 4m = 0$$


$$I_0 = \frac{V_2}{1k}$$

$$\boxed{I_0 = 7m(A)}$$

$$\begin{bmatrix} -\frac{1}{1k} - \frac{1}{2k} & \frac{1}{2k} \\ \frac{1}{2k} & -\frac{1}{1k} - \frac{1}{2k} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2m \\ -10m \end{bmatrix}$$

$$\Rightarrow \text{(MATLAB)} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} 1 \\ 7 \end{pmatrix} (V)$$

3.36

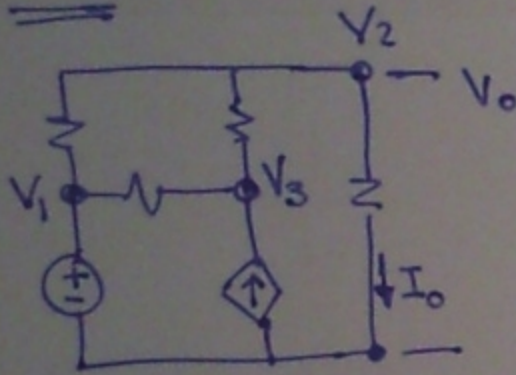

$$V_1 = 12$$

$$\frac{V_1 - V_2}{1k} + \frac{V_3 - V_2}{1k} + \frac{0 - V_2}{1k} = 0$$

$$\frac{V_1 - V_3}{1k} + 2I_0 + \frac{V_2 - V_3}{1k} = 0$$

$$I_0 = \frac{V_2}{1k}$$

$$\boxed{V_0 = V_2 = 12(V)}$$

$$\rightarrow A \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = b$$

$$A = \begin{bmatrix} \frac{1}{1k} & -\frac{1}{1k} - \frac{1}{1k} - \frac{1}{1k} & \frac{1}{1k} \\ 1 & 0 & 0 \\ \frac{1}{1k} & \frac{1}{1k} + 2 & \frac{1}{1k} - \frac{1}{1k} - \frac{1}{1k} \end{bmatrix}$$

$$b = \begin{bmatrix} 0 \\ 12 \\ 0 \end{bmatrix} \Rightarrow \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{bmatrix} 12 \\ 12 \\ 24 \end{bmatrix}$$

3.65



$$I_1 - I_2 = 2m$$

$$I_3 - I_4 = -4m$$

$$I_1 2k + I_2 1k + I_3 2k + I_4 1k = 0$$


$$I_1 2k + I_2 1k - 4 + 6 = 0$$

$$V_0 = I_2 1k + I_3 2k$$

$$\rightarrow \begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & -1 \\ 2k & 1k & 2k & 1k \\ 2k & 1k & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} -2m \\ -4m \\ 0 \\ -2 \end{bmatrix} \Rightarrow \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} -\frac{4}{3}m \\ \frac{2}{3}m \\ \frac{2}{3}m \\ \frac{10}{3}m \end{bmatrix}$$

$$\Rightarrow \boxed{V_0 = -\frac{2}{3}(V)}$$

3.66

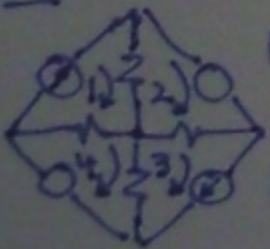

$$I_1 = 6m$$

$$(I_2 - I_1) 1k + 4 + (I_2 - I_3) 2k = 0$$

$$I_3 = 4m$$

$$(I_4 - I_1) 2k + (I_4 - I_3) 1k + 6 = 0$$

$$V_0 = (I_1 - I_2) 1k + (I_4 - I_3) 1k$$

$$\rightarrow \begin{bmatrix} 1 & 0 & 0 & 0 \\ -1k & 1k + 2k & -2k & 0 \\ 0 & 0 & 1 & 0 \\ -2k & 0 & -1k & 2k + 1k \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 6m \\ -4 \\ 4m \\ -6 \end{bmatrix} \Rightarrow \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 6m \\ 3.33m \\ 4m \\ 3.33m \end{bmatrix}$$

$$\Rightarrow \boxed{V_0 = 2(V)}$$

Pr. 1.37 $P = 6 I_x$, where by KCL $I_x + 2 = 2I_x$.

$\Rightarrow I_x = 2A \Rightarrow P = 12W$, Absorbed

Pr. 1.43 Perform a power balance:

$P_1 = 6 \times 8 = +48$, $P_2 = 4 \times 10 = +40$, $P_3 = I_o \times 6$

$P_4 = 2 \times 16 = +32$, $P_5 = 6 \times 1 = +6$, $P_6 = 8 \times 3 = 24$

Source 1 = $-24 \times 6 = -144$, Source 2 $-3 \times 4 I_x = -3 \times 8 = -24$
(all in W). $\Rightarrow I_o = 18/6 = 3(A)$.

Pr. 2.35 $R_{eff} = \left(\frac{4}{4R} + \frac{1}{4R} \right)^{-1} = \frac{4R}{5}$, $100 \frac{S}{4R} = 50 \Rightarrow R = \frac{2.5}{(A)}$

Pr. 2.43 $P = I \cdot 2V_x$

KVL 1: $-20 + 10kI + 2V_x + 5kI - 10 + 2kI + 3kI + 10kI = 0$

KVL 2: $-V_x - 10 + 2kI + 3kI = 0$

$\Rightarrow V_x = -3.75 (V)$ $\left\{ \Rightarrow P = -9.375 \text{ mW} \text{ absorbed} \right.$
 $I = 1.25 \text{ mA}$ $\left. (\Rightarrow 9.375 \text{ mW} \text{ supplied}) \right.$

Pr. 2.46 KVL1: $-20 + 10I + 20I + V_2 = 0$ $\left\{ \Rightarrow I = 2, V_2 = -40 (V) \right.$
KVL2: $-V_1 + 20I + V_2 = 0$

Pr. 2.48 Find the node voltage first: $12 \text{ mA} \times (12k \parallel 12k \parallel 6k)$
 $= 36V$

$\Rightarrow I_o = V/R = -36/12k = -3 \text{ mA}$ (notice current orientation)

Pr. 2.58 Top half: $R_{eff} = 4 \parallel 0 \parallel 6 = 0$

Bottom half: $R_{eff} = 8 \parallel 0 \parallel (10+2) = 0$

$\Rightarrow R_{AB} = 0$

4.11 Assuming an ideal op-amp in Fig. P4.11, determine the value of R_X that will produce a voltage gain of 26.

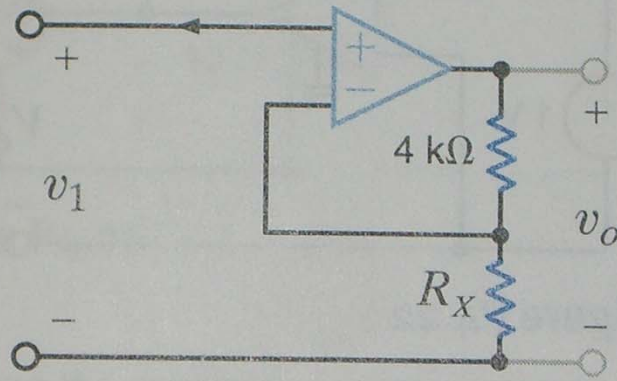


Figure P4.11

4.25 Determine the relationship between v_1 and i_o in the circuit shown in Fig. P4.25.

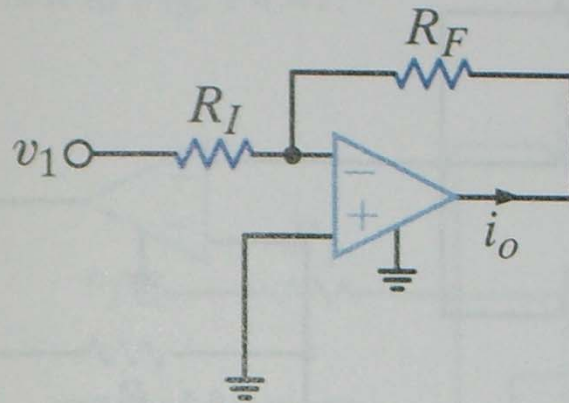


Figure P4.25

5.20 Use superposition to find V_o in the network in Fig. P5.20.

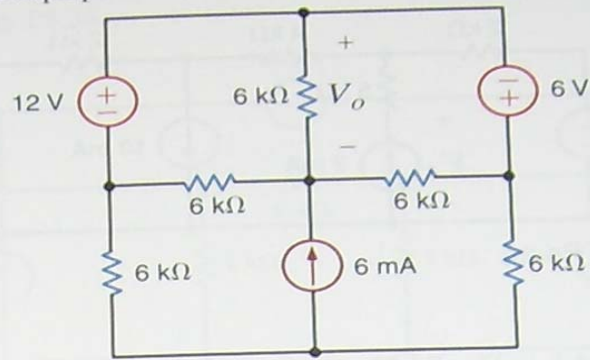


Figure P5.20

5.33 Use Thévenin's theorem to find I_o in the circuit using Fig. P5.33.

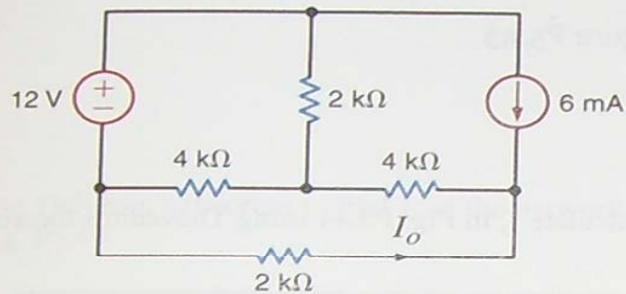


Figure P5.33

5.52 Use Norton's theorem to find I_o in the circuit in Fig. P5.52.

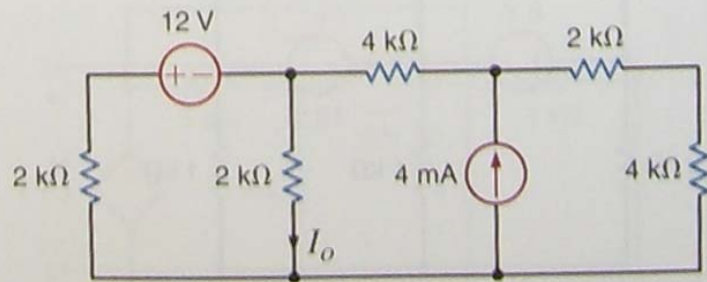


Figure P5.52

5.49 Given the linear circuit in Fig. P5.49, it is known that when a 2-k Ω load is connected to the terminals A–B, the load current is 10 mA. If a 10-k Ω load is connected to the terminals, the load current is 6 mA. Find the current in a 20-k Ω load.

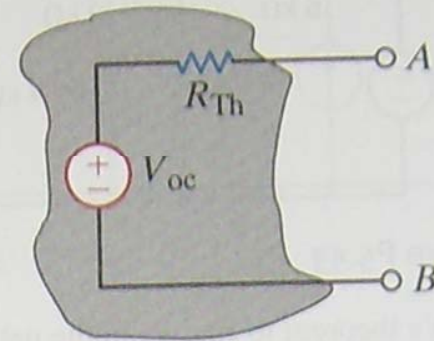


Figure P5.49

5.87 Find V_o in the network in Fig. P5.87 using source transformation.

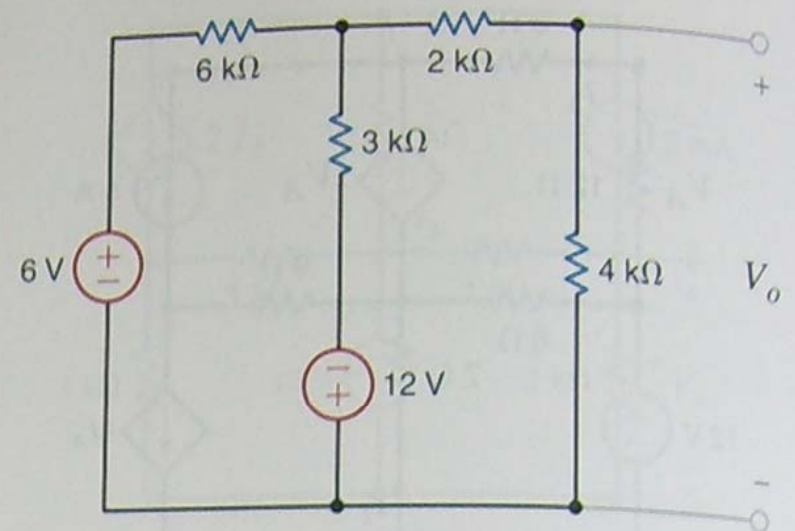


Figure P5.87

4.11 At the inverting node of the op-amp: $\frac{v_o - v_-}{4k} + \frac{0 - v_-}{R_x} = 0$


Under the ideal op-amp assumption $v_- = v_+ = v_1$


$\therefore v_o = 4k \left(\frac{1}{4k} + \frac{1}{R_x} \right) v_1 = 26 v_1 \Rightarrow \frac{4k}{R_x} = 25 \Rightarrow R_x = 160 \Omega$


4.25 Ideal Op amp: $v_- = v_+ = 0 \Rightarrow \frac{v_1 - 0}{R_1} + i_o = 0 \Rightarrow i_o = -\frac{v_1}{R_1}$

(For a constant voltage v_1 , this becomes a constant current supply to a variable load R_F)

5.20 Superposition: eliminate all sources except one at a time and add up the results.

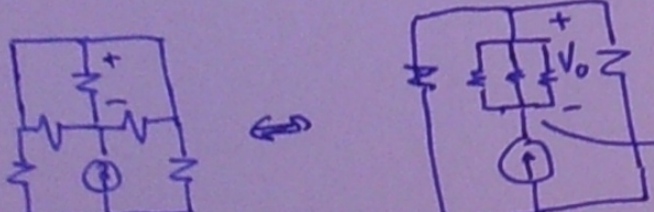1)  $\Rightarrow R_{\text{eff}} = 6k \parallel 6k \parallel 6k = 2k$
 $\Rightarrow v_{o1} = -6m \cdot 2k = -12V$

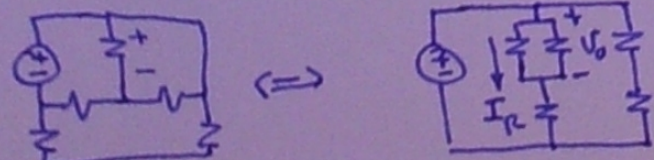
2)  $I_R = \frac{12}{9k} \Rightarrow v_{o2} = I_R \cdot 3k = 4V$

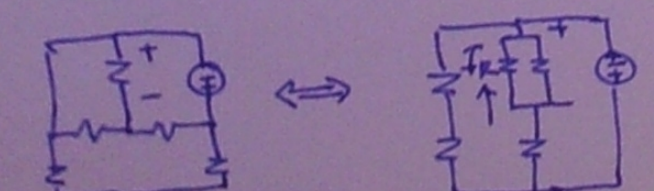3)  $I_R = \frac{6}{9k} \Rightarrow v_{o3} = -\frac{6}{9k} \cdot 3k = -2V$

$\therefore v_o = v_{o1} + v_{o2} + v_{o3} \Rightarrow v_o = -10V$

5.33

Find the Thevenin equivalent of

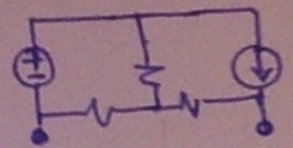


E.g. use loop analysis I_1 I_2

$$\begin{cases} -12 + 2k(I_1 - I_2) + 4kI_1 = 0 \\ I_2 = 6m \end{cases} \Rightarrow I_1 = 4m$$

$$\Rightarrow V_{oc} = -I_1 4k - I_2 4k = -40 (v)$$

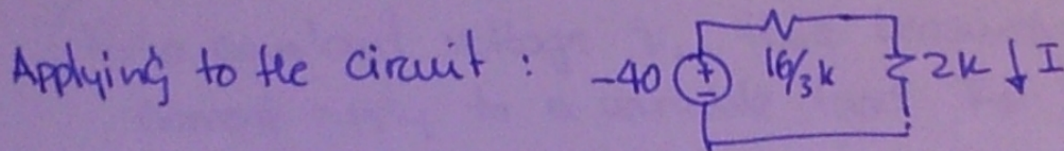
$$\Rightarrow R_{TH} : \text{Circuit diagram} = \left(\frac{1}{2k} + \frac{1}{4k} \right)^{-1} + 4k = \frac{16}{3} k(\Omega)$$



$$I = \frac{-40}{2k + \frac{16}{3}k} = -\frac{60}{11} m(A) = -5.45 mA$$


5.52

Find the Norton equivalent of

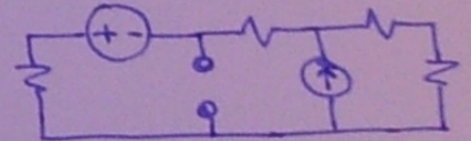

→ short the terminals to compute I_{sc}

e.g. loop analysis:

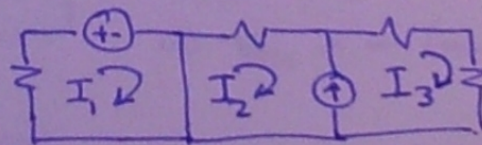

$$I_{sc} = I_1 - I_2$$

$$2kI_1 + 12 = 0$$


$$4kI_2 + 2kI_3 + 4kI_3 = 0$$

$$I_3 - I_2 = 4m$$

e.g. MATLAB

$$\Rightarrow I_{sc} = -3.6 m(A)$$
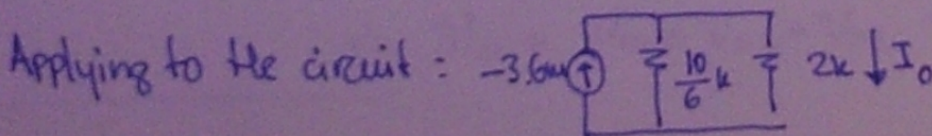
$$\Rightarrow R_{TH} : \text{Circuit diagram} \quad R_{TH} = 2k \parallel (2k + 4k + 4k) = \frac{10}{6} k(\Omega)$$



Using current division

$$I_0 = -3.6m \frac{10/6 k}{10/6 k + 2k} = -\frac{36}{22} m$$

$$I_0 = -1.64 mA$$

549



1. $R_L = 2k$ $I = 10mA = \frac{V_{oc}}{R_{TH} + 2k}$

2. $R_L = 10k$ $I = 6mA = \frac{V_{oc}}{R_{TH} + 10k}$



$\Rightarrow R_{TH} = 10k (\Omega)$

$\Rightarrow V_{oc} = 120 (v)$

\therefore for $R_L = 20k$,

$I = \frac{120}{10k + 20k} = 4mA$

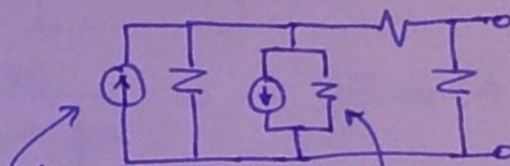
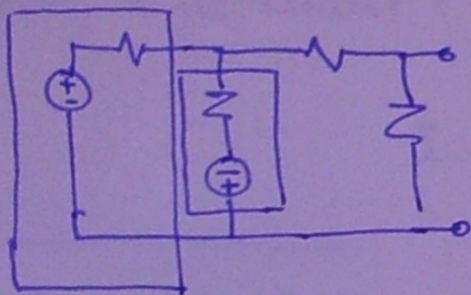
5.87 **SOURCE** Transformations as indicated




$I_1 = \frac{6}{6k} = 1mA$
 $R_1 = 6k$

$I_2 = \frac{12}{3k} = 4mA$
 $R_2 = 3k$

Rearranging

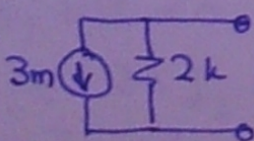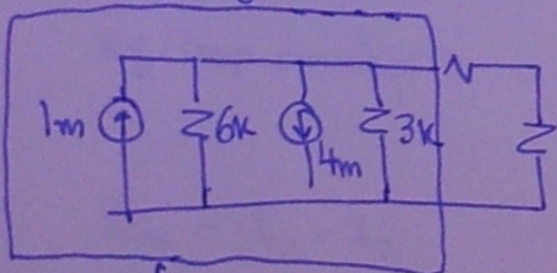

$V = \frac{3mA \cdot 2k}{3}$

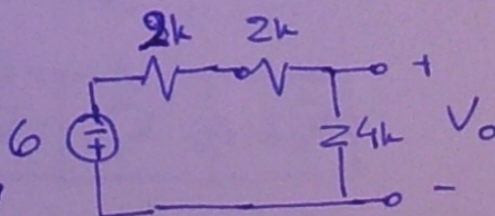

Applying Voltage division, $V_o = -6 \cdot \frac{4k}{2k + 2k + 4k} = -\frac{24}{8}$

$\Rightarrow V_o = -3 (v)$

- 6.13 The current flowing through a $5\text{-}\mu\text{F}$ capacitor is shown in Fig. P6.13. Find the energy stored in the capacitor at $t = 1.4\text{ ms}$, $t = 3.3\text{ ms}$, $t = 4.3\text{ ms}$, $t = 6.7\text{ ms}$, and $t = 8.5\text{ ms}$.

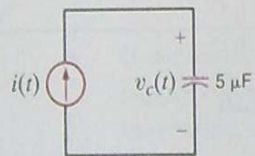
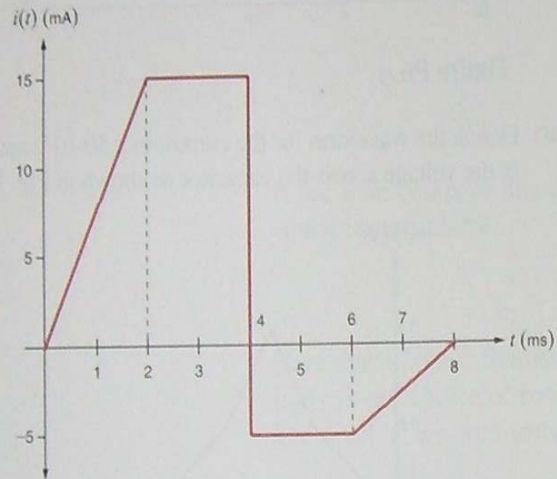


Figure P6.13

- 6.55 Determine C_T in the circuit in Fig. P6.55 if all capacitors in the network are $6\text{ }\mu\text{F}$.

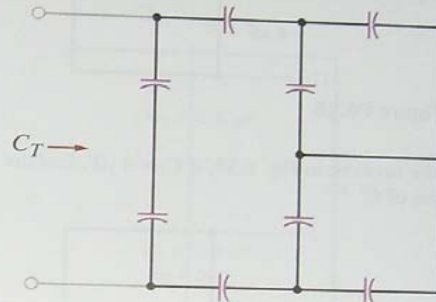


Figure P6.55

- 6.56 Find C_T in the circuit in Fig. P6.56 if all capacitors are $6\text{ }\mu\text{F}$.

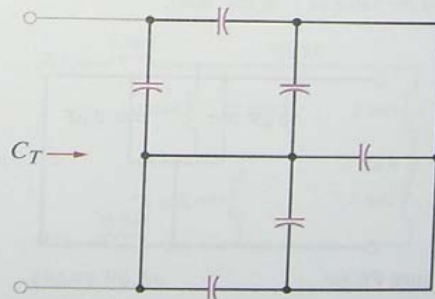


Figure P6.56

- 6.27 The voltage across a 2-H inductor is given by the waveform shown in Fig. P6.27. Find the waveform for the current in the inductor.

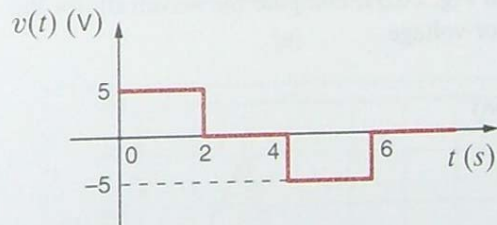


Figure P6.27

- 6.47 Calculate the energy stored in both the inductor and the capacitor shown in Fig. P6.47.

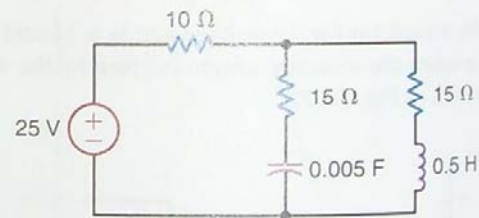


Figure P6.47

- 7.46 Find $i_o(t)$ for $t > 0$ in the network in Fig. P7.46 using the step-by-step method.


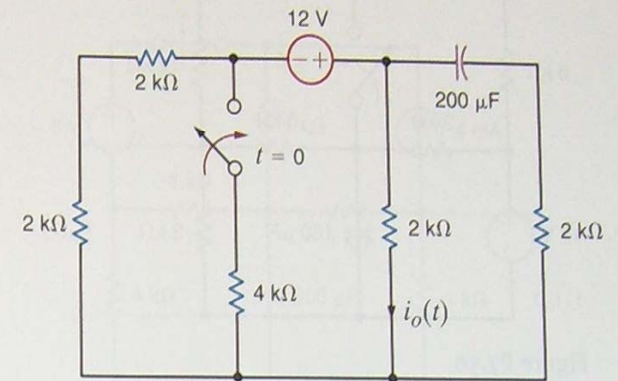


Figure P7.46

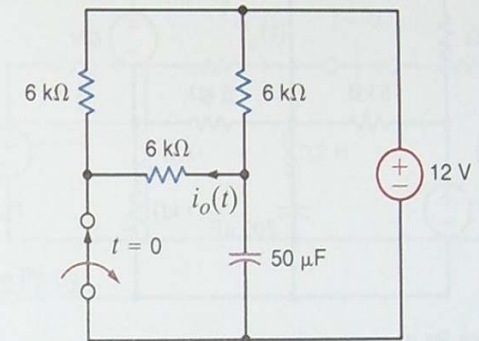- 7.47 Use the step-by-step method to find $i_o(t)$ for $t > 0$ in the network in Fig. P7.47.



ECE 202 HW#3 SOLUTIONS

6.13 $i = C \frac{dV}{dt}$ or $V(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = V(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$

\therefore for $t \in [0, 2m]$, $V(t) = \frac{1}{5\mu} \int_0^t \frac{15}{2} \tau d\tau = \underline{7.5E5 t^2}$ (in V)

at $t = 2ms$, $V(2m) = 3V$

for $t \in [2m, 4m]$ $V(t) = V(2m) + \frac{15m}{5\mu} (t - 2m) = \underline{3 + 3E3(t - 2m)}$

at $t = 4ms$, $V(4m) = 9V$

for $t \in [4m, 6m]$ $V(t) = V(4m) - \frac{5m}{5\mu} (t - 4m) = \underline{9 - 1E3(t - 4m)}$

at $t = 6m$, $V(6m) = 7V$

for $t \in [6m, 8m]$ $V(t) = V(6m) + \frac{1}{5\mu} \left[\frac{5m}{2m} \frac{(t - 6m)^2}{2} - 5m(t - 6m) \right]$
 $= 7 + \frac{1}{4} E6(t - 6m)^2 - 1E3(t - 6m)$

at $t = 8$, $V(8) = 6V$

The energy stored in the capacitor is $\frac{1}{2} CV^2$, so

at $t = 1.4ms$, $V(1.4ms) = 1.47 \Rightarrow E = \frac{1}{2} 5\mu \cdot 1.47^2 = \underline{5.4 \mu J}$


$t = 3.3ms$, $V(3.3ms) = 6.9 \Rightarrow \underline{E = 119 \mu J}$

$t = 4.3ms$, $V(4.3ms) = 8.7 \Rightarrow \underline{E = 189 \mu J}$

$t = 6.7ms$, $V(6.7ms) = 6.42 \Rightarrow \underline{E = 103 \mu J}$

$t = 8.5ms$, $V(8.5ms) = 6 \Rightarrow \underline{E = 90 \mu J}$

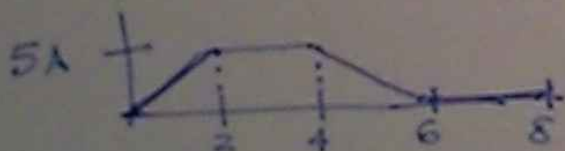6.27 $V(t) = L \frac{di}{dt}$ or $i = \frac{1}{L} \int v \Rightarrow$ the graph for $i(t)$ is




To find the peak, we note that the slope is $\frac{v}{L} = \frac{5}{2}$ so
 $\frac{1}{2} \int_0^2 5 dt = 5 (A)$

6.47

$$V_C = \frac{15}{15+10} 25 = 15(V) \Rightarrow E_C = \frac{1}{2} C V^2 = \frac{1}{2} \cdot 5 \cdot 10^{-3} \cdot 15^2 = 0.56 J$$


$$I_L = \frac{25(V)}{(10+15)(\Omega)} = 1(A) \Rightarrow E_L = \frac{1}{2} L I^2 = \frac{1}{2} \cdot 0.5 \cdot 1^2 = 0.25 J$$

6.55

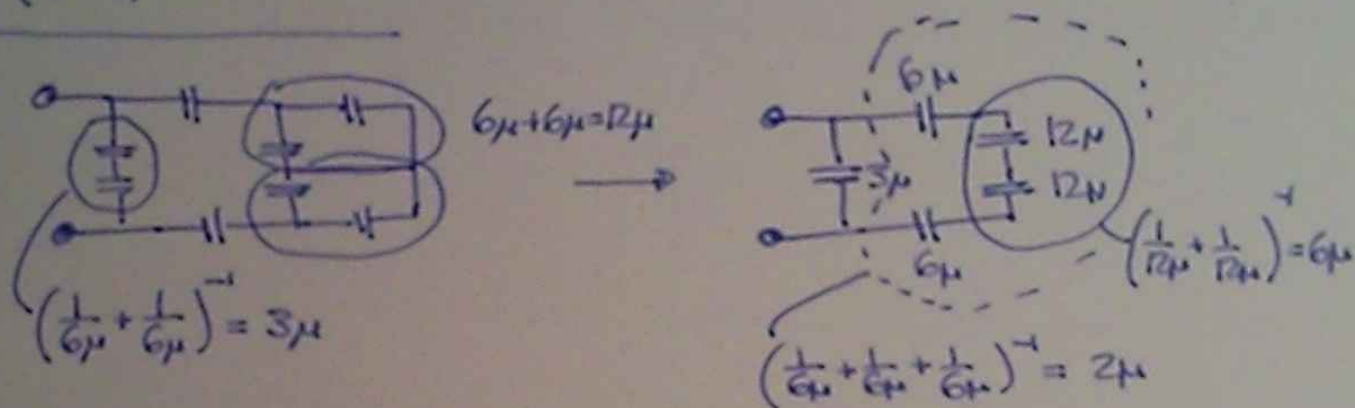

$$\Rightarrow C_{\text{eff}} = 3\mu + 2\mu = \underline{\underline{5\mu F}}$$

6.56

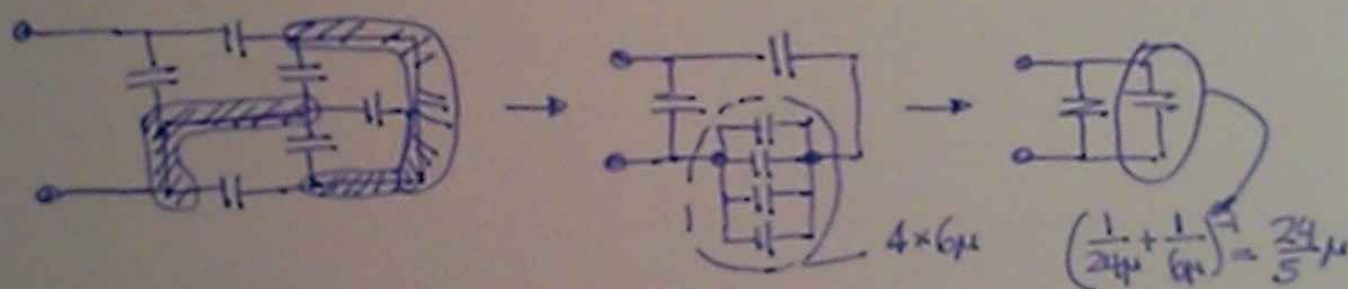

$$\Rightarrow C_{\text{eff}} = \frac{24}{5}\mu + 6\mu = \underline{\underline{\frac{54}{5}\mu F}}$$

7.46 The step-by-step method for discontinuous variables (i.e. other than capacitor voltages and inductor currents) can be described as follows

I. Solve for V_C (or I_L) & Replace Cap (or Ind.) by a voltage (or current) source $V_C(t)$ (or $I_L(t)$) and solve the resulting circuit.

II. 1) Find $V_C(0^-)$ (or $I_L(0^-)$) with the $t < 0$ -circuit.

2) Set $V_C(0^+) = V_C(0^-)$ (or $I_L(0^+) = I_L(0^-)$) and substitute the capacitor with a voltage source $V_C(0^+)$ (or the inductor with a current source $I_L(0^+)$).


3) Compute the initial condition for the variable of interest, say x , such that $x(0^+) = \text{value for the } t > 0 \text{-circuit}$ (with the caps replaced by voltage sources).


4) Compute $x(\infty)$ for the $t > 0$ circuit


5) Compute R_{TH} as seen by the capacitor (or inductor) for the $t > 0$ circuit.


6) $x(t) = x(\infty) + [x(0) - x(\infty)] e^{-t/\tau}$; $\tau = R_{TH}C$ (or R_{TH}/L).

For our problem,

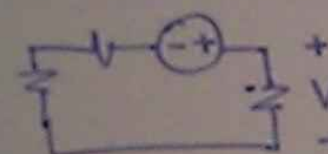1) $t < 0$  $V_0 = \frac{2k}{6k} 12 = 4V$

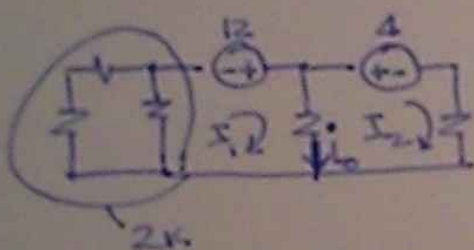2) $t > 0$ 
$$\begin{aligned} I_1 \cdot 2k - 12 + 2k(I_1 - I_2) &= 0 \\ 4 + 2kI_2 + 2k(I_2 - I_1) &= 0 \\ \Rightarrow I_1 &= \frac{10}{3} \text{ mA}, I_2 = \frac{4}{6} \text{ mA} \\ \Rightarrow \underline{i_0(0^+) = I_1 - I_2 = \frac{8}{3} \text{ mA}} \end{aligned}$$

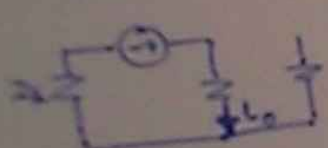3) $t > 0$  $\Rightarrow i_0(\infty) = \frac{12}{4k} = 3 \text{ mA}$

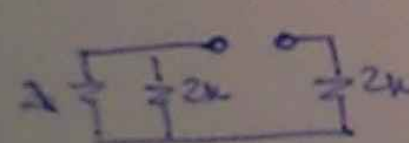
4) $t > 0$  $\Rightarrow R_{TH} = \left(\frac{1}{2k} + \frac{1}{2k}\right)^{-1} + 2k = 3k \Omega$

5) $i(t) = 3 \text{ mA} + \left(\frac{8}{3} \text{ mA} - 3 \text{ mA}\right) e^{-t/0.60} \text{ (A)}$

where $0.60 \text{ ms} = \tau = R_{TH} \cdot C = 3k \cdot 200\mu = 600 \text{ ms}$


7.47
=

$t < 0$

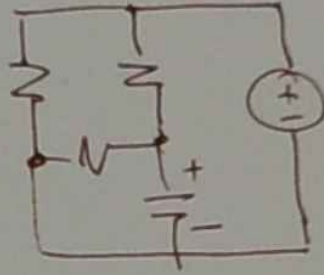

$$V_c(0) = \frac{(12)(6k)}{6k + 6k} = 6 \text{ (v)}$$

$t > 0$

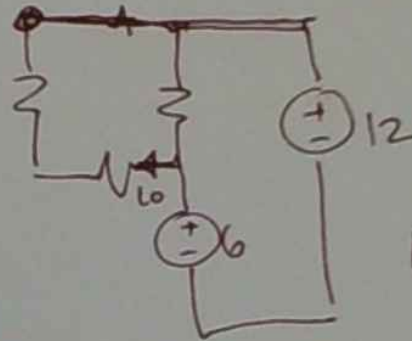


$$I_o(0) = -\frac{(12-6)}{6k+6k}$$

$$= \frac{1}{2} \text{ mA}$$

$t > 0 \quad I_o(\infty) = 0$
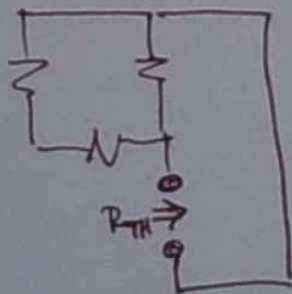
$$\Rightarrow I_o(t) = \frac{1}{2} \text{ mA} e^{-\frac{t}{\tau}} \quad T = R_{TH}C = 200 \text{ms} = 0.2 \text{ s}$$



$$R_{TH} = 6k \parallel (6k + 6k) = 4k$$

$$C = 50\mu \Rightarrow \tau = 200 \text{ms}$$

8.28 Calculate $v_C(t)$ in Fig. P8.28.

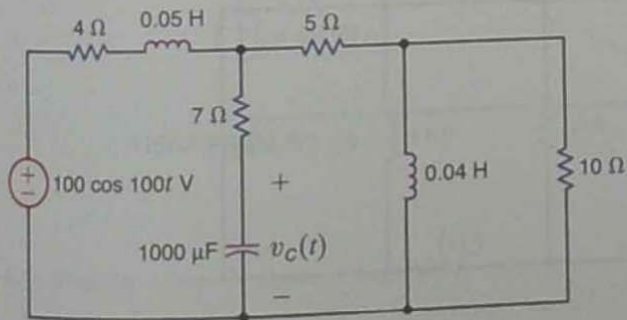


Figure P8.28

8.30 Find $v_o(t)$ and $i_o(t)$ in Fig. P8.30.

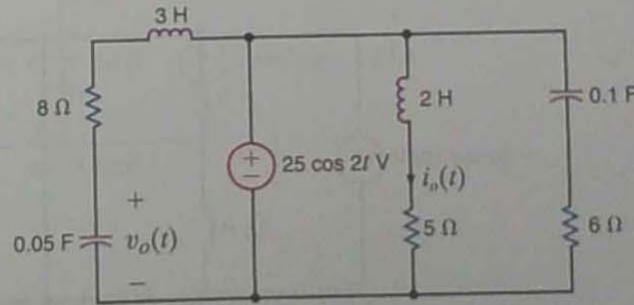


Figure P8.30

8.48 In the network in Fig. P8.48, $I_o = 4 \angle 0^\circ$ A. Find I_x .

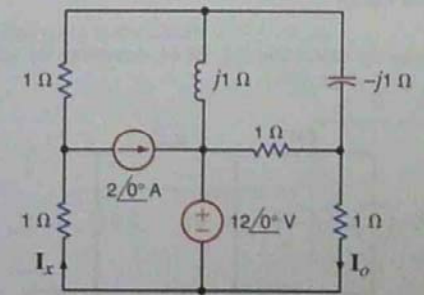


Figure P8.48

8.71 Use loop analysis, to find V_o in the circuit in Fig. P8.71.

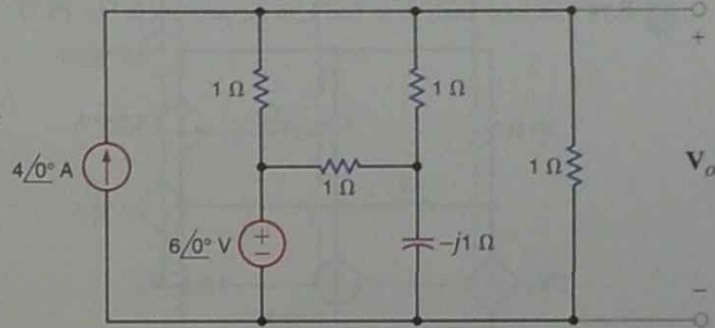


Figure P8.71

8.47 In the network in Fig. P8.47, V_o is known to be $4 \angle 45^\circ$ V. Find Z .

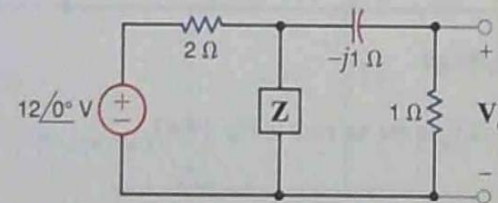


Figure P8.47

9.28 Determine the average power absorbed by the 2-k Ω output resistor in Fig. P9.28.

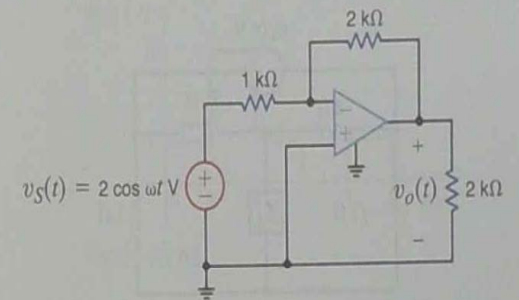


Figure P9.28

9.8 Find the instantaneous power supplied by the source in the network in Fig. P9.8.

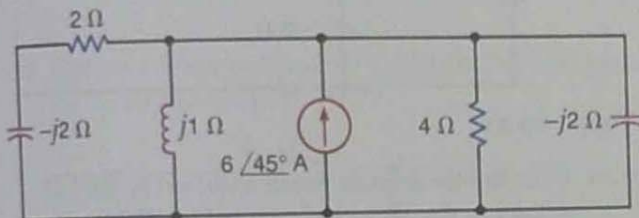


Figure P9.8

9.12 Find the average power absorbed by the 2- Ω resistor in the network in Fig. P9.12 and the total power supplied.

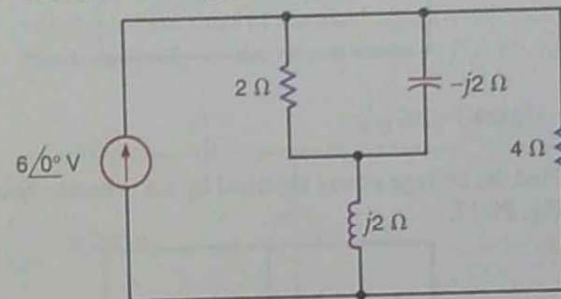


Figure P9.12

9.29 Determine the impedance Z_L for maximum average power transfer and the value of the maximum power transferred to Z_L for the circuit shown in Fig. P9.29.


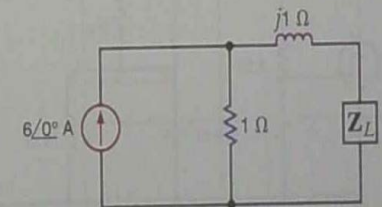


Figure P9.29

EE E 202 HW4 SOLUTIONS

8.28

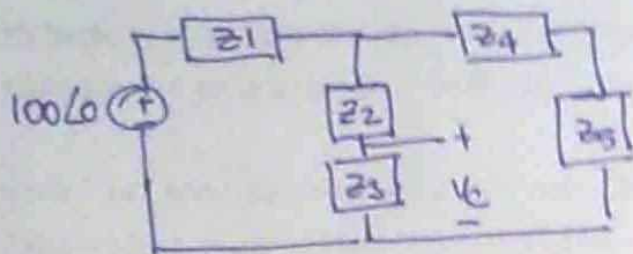

where: $z_1 = 4 + 0.05j100$

$z_2 = 7$

$z_3 = 1/j100 \cdot 1000 E-6$

$z_4 = 5$

$z_5 = \left(\frac{1}{0.04j100} + \frac{1}{10} \right)^{-1}$

Then, $V_c = z_3(I_1 - I_2)$

$$-100\angle 0 + z_1 I_1 + (z_2 + z_3)(I_1 - I_2) = 0$$

$$(z_4 + z_5) I_2 + (z_3 + z_2)(I_2 - I_1) = 0$$

$$\Rightarrow \begin{bmatrix} z_1 + z_2 + z_3 & -z_3 - z_2 \\ -z_3 - z_2 & z_2 + z_3 + z_4 + z_5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \end{bmatrix}$$


$$\Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 8.06 - 4.01j \\ 4.19 - 6.07j \end{bmatrix} \Rightarrow V_c = 20.6 - 38.7j$$

$$= 43.8 \angle -62^\circ$$

$$\Rightarrow V_c(t) = 43.8 \cos(100t - 62^\circ)$$

$\hookrightarrow -1.08 \text{ rad}$

8.30

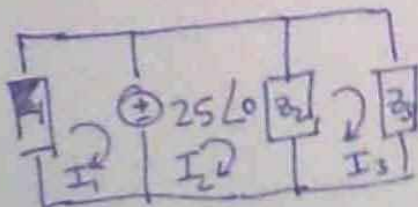

where: $z_1 = 8 + 3j2 + \frac{1}{j2 \cdot 0.05}$

$z_2 = 2j2 + 5$

$z_3 = \frac{1}{j0.12} + 6$

$$V_0 = \frac{1}{j2 \cdot 0.05} (-I_1) \quad \left| \begin{array}{l} + z_1 I_1 + 25\angle 0 = 0 \\ \rightarrow \end{array} \right.$$

$$I_0 = I_2 - I_3 = 25\angle 0 \cdot \frac{1}{z_2}$$


$$V_0 = 12.5 - 25j = 28 \angle -63.4^\circ$$

$$I_0 = 3.05 - 2.44j = 3.9 \angle -38.7^\circ$$

$$V_0(t) = 28 \cos(2t - 63.4^\circ)$$

$$I_0(t) = 3.9 \cos(2t - 38.7^\circ)$$

8.48

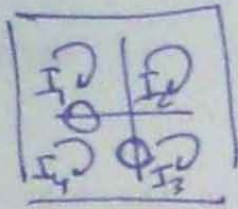

$$-I_1 + I_4 = 2 \angle 0$$

$$I_2(-j) + (I_2 - I_3)1 + (I_2 - I_1)j = 0$$

CAN SIMPLIFY
to $I_x = I_3$

from problem data

$$(I_3 - I_2)1 + I_3 \cdot 1 - 12 \angle 0 = 0$$

$$I_1 \cdot 1 + (I_1 - I_2)j + 12 \angle 0 + I_4 \cdot 1 = 0$$

$$I_x = I_4$$

$$\Rightarrow \begin{bmatrix} -1 & 0 & 0 & 1 \\ -j & -j+1+j & -1 & 0 \\ 0 & -1 & 1+1 & 0 \\ 1+j & -j & 0 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ 12 \\ -12 \end{bmatrix} \Rightarrow \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 2.59 + 3.65j \\ 4.71 - 5.18j \\ 8.35 - 2.59j \\ -0.59 + 3.65j \end{bmatrix}$$

$$\Rightarrow I_x = 3.69 \angle 99.2^\circ$$

NOTE: - Real part $< 0 \Rightarrow$
180° correction is needed

- I_3 is NOT as given
(obviously a typo)

8.49

$$V_o = V_z \cdot \frac{1}{1-j} \quad (V_z: \text{voltage across } z)$$


$$V_z = V_s \cdot \frac{z \parallel (1-j)}{2 + (z \parallel (1-j))} \quad (V_s: \text{voltage of source})$$

$$\Rightarrow 12(z \parallel (1-j)) = (1-j)(4 \angle 45^\circ)(2 + (z \parallel (1-j)))$$

$$\Rightarrow z \parallel (1-j) = \frac{2(1-j)(4 \angle 45^\circ)}{12 - (1-j)(4 \angle 45^\circ)} = 1.78$$

$$\Rightarrow \left(\frac{1}{z} + \frac{1}{1-j}\right)^{-1} = 1.78 \Rightarrow \boxed{z = 0.24 + 1.97j = 1.98 \angle 83^\circ}$$

8.71

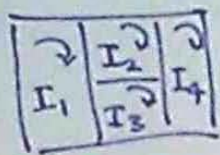

$$I_1 = 4 \angle 0$$

$$(I_2 - I_1) \cdot 1 + (I_2 - I_4) \cdot 1 + (I_2 - I_3) \cdot 1 = 0$$

$$-6 \angle 0 + (I_3 - I_2) \cdot 1 + (I_3 - I_4) \cdot (-j) = 0$$

$$(I_4 - I_3) \cdot (-j) + (I_4 - I_2) \cdot 1 + I_4 \cdot 1 = 0$$

$$V_o = I_4 \cdot 1$$

$$\Rightarrow \begin{bmatrix} 1 & 0 & 0 & 0 \\ -1 & 1+1 & -1 & -1 \\ 0 & -1 & 1-j & j \\ 0 & -1 & j & -j+1+1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 4 \\ 0 \\ 6 \\ 0 \end{bmatrix} \Rightarrow \begin{matrix} I_1 & 4 \\ I_2 & 5.29 + 0.82j \\ I_3 & 7.18 + 3.29j \\ I_4 & 4.71 - 0.82j \end{matrix}$$

$$\Rightarrow V_o = 4.71 - 0.82j = 4.78 \angle -9.9^\circ$$

$$\underline{9.8} \quad Z_{\text{eff}} = \left(\frac{1}{-j2} + \frac{1}{4} + \frac{1}{j1} + \frac{1}{2-j2} \right)^{-1} = 1.6 + 0.8j = 1.79 \angle 26.6^\circ$$

$$\Rightarrow V_s = I_s Z_{\text{eff}} = (6 \angle 45^\circ)(1.79 \angle 26.6^\circ) = 10.73 \angle 71.6^\circ$$

$$\Rightarrow \text{Source Power } P(t) = -V_s(t) i_s(t) \quad (- : \text{supplied power})$$

$$= -6 \cos(\omega t + 45^\circ) \cdot 10.73 \cos(\omega t + 71.6^\circ) \quad (\text{W})$$

Notes: 1. $P(t)$ is not represented by a phasor, it is a product of $\cos \omega t$ - terms.

2. The product of the phasors V_s and I_s is not Power

3. ω here is not given

4. The average power is $P_{\text{av}} = \frac{|V_s||I_s|}{2} \cos(\angle V_s - \angle I_s)$

$$\Rightarrow P_{\text{av}} = \frac{1}{2} 6 \times 10.73 \cos(26.6^\circ) = 28.71 \text{ (W)}$$

$$9.8 \quad z_{\text{eff}} = 1.79 \angle 26.6$$

$$V_s = (6 \angle 45) \cdot (1.79 \angle 26.6) = 10.73 \angle 71.6$$

$$P(t) = V(t)I(t) = 6 \cos(\omega t + 45) \cdot 10.73 \cos(\omega t + 71.6)$$

$$= 64.4 \cos(\omega t + 45) \cos(\omega t + 71.6)$$

Note $V \cdot I$ the product of phasors is not P .

$$P_{\text{AV}} = \frac{1}{2} 64.4 \cos(45 - 71.6)$$

$$= \frac{1}{2} 64.4 \cos(26.6) = 28.79$$

$$P_R = \frac{1}{2} \cdot 10.73^2 \cdot \frac{1}{4} = 14.39$$

2k

$$\text{OPAMP} : V_o = - \frac{2k}{1k} V_s$$

$$I_o = V_o / 2k$$

$$\frac{1}{2} |V_o| |I_o| \cdot \cos(\angle V_o - \angle I_o)$$

$$= \frac{1}{2} \left| \frac{2k}{1k} \right| |V_s| \cdot \left| \frac{2k}{1k} V_s \right| \cdot \frac{1}{2k} \quad |V_o| = 2$$

$$= \frac{1}{2} |2V_s| |2V_s| \cdot \frac{1}{2k}$$

$$\frac{1}{2} 4 \cdot 4 \cdot \frac{1}{2k} = \frac{1}{1k} \text{ (w)} = 1 \text{ mW}$$

$$9.12 \quad Z_{TOT} = \left(\frac{1}{4} + \frac{1}{Z_1} \right)^{-1} = \dots = 0.92 + 0.62j$$

$$Z_1 = j2 + \left(\frac{1}{2} + \frac{1}{-2j} \right)^{-1} = 1 + j$$

Source Voltage: $V_s = I_s Z_{TOT} = 5.54 + 3.69j = 6.66 \angle 33.7^\circ$

Avg. Pow. source: $P_s = -\frac{1}{2} \cdot |V_s| |I_s| \cdot \cos(\angle V_s - \angle I_s) = -\frac{1}{2} (6.66)(6) \cos(33.7^\circ)$
 $= -16.6 \text{ (W)}$

Avg. Pow. 4Ω: $P_{4\Omega} = \frac{1}{2} |V_{4\Omega}| |I_{4\Omega}| \cos 0^\circ = \frac{1}{2} |V_s| \left| \frac{V_s}{4} \right| = 5.54 \text{ (W)}$

RESISTANCE

$$\Rightarrow \text{Avg. Pow. } 2\Omega = P_{2\Omega} = -(P_s + P_4) = \boxed{11.08 \text{ (W)}}$$

Alt. Computation:

$$V_{2\Omega} = V_s \frac{(1/2 - 1/2j)^{-1}}{Z_j + (1/2 - 1/2j)^{-1}} = 3.69 - 5.54j$$


$$I_{2\Omega} = V_{2\Omega} / R$$

$$P_{2\Omega} = \frac{1}{2} |V_{2\Omega}| |I_{2\Omega}| \cos 0 = 11.08 \text{ (W)}$$

9.28 For an ideal opamp, $V_o = -\frac{2k}{1k} V_s \Rightarrow I_o = V_o \cdot \frac{1}{2k}$

Avg. Pow: $P = \frac{1}{2} |V_o| |I_o| \cdot \cos 0 = \frac{1}{2} \cdot 4 \cdot 4/2k = \boxed{4 \text{ m(W)}}$
 RESISTIVE LOAD

9.29 Apply source transformation:

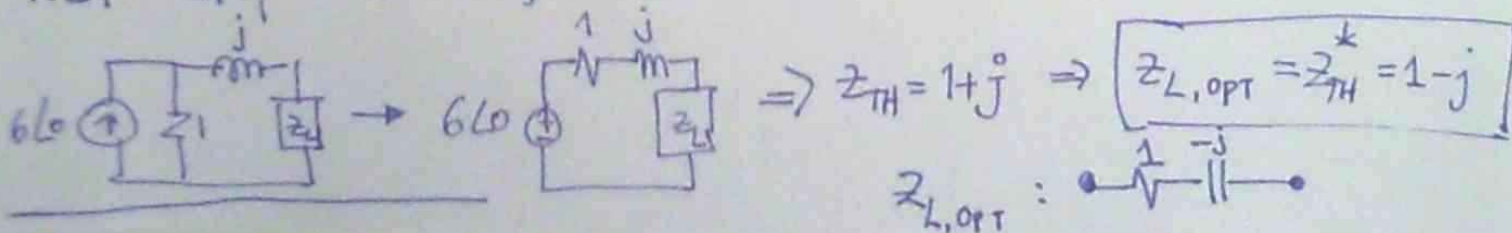

- 12.43** A variable-frequency voltage source drives the network in Fig. P12.43. Determine the resonant frequency, Q , BW, and the average power dissipated by the network at resonance.

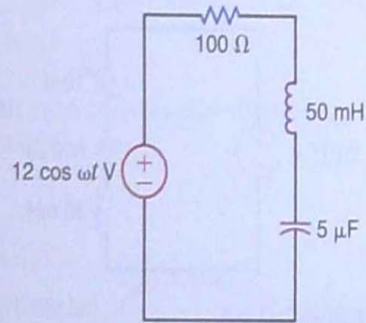


Figure P12.43

- 12.44** In the network in Fig. P12.44, the inductor value is 10 mH, and the circuit is driven by a variable-frequency source. If the magnitude of the current at resonance is 12 A, $\omega_0 = 1000$ rad/s, and $L = 10$ mH, find C , Q , and the bandwidth of the circuit.

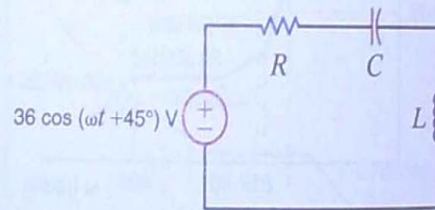


Figure P12.44

- 12.26** Sketch the magnitude characteristic of the Bode plot for the transfer function

$$\mathbf{H}(j\omega) = \frac{+6.4(j\omega)}{(j\omega + 1)(-\omega^2 + 8j\omega + 64)}$$

- 12.27** Find $\mathbf{H}(j\omega)$ if its magnitude characteristic is shown in Fig. P12.27.

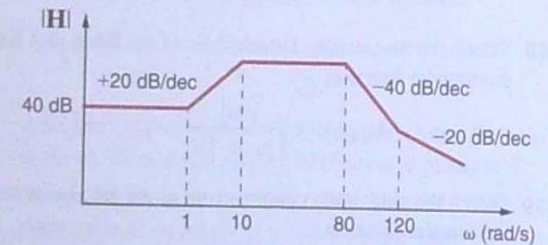


Figure P12.27

- 12.8** Find the transfer impedance $V_o(s)/I_s(s)$ for the network shown in Fig. P12.8.

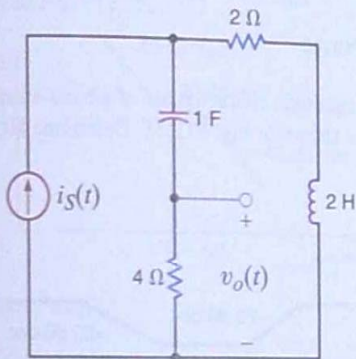


Figure P12.8

- 12.9** Draw the Bode plot for the network function

$$\mathbf{H}(j\omega) = \frac{j\omega^4 + 1}{j\omega^20 + 1}$$

- 12.10** Draw the Bode plot for the network function

$$\mathbf{H}(j\omega) = \frac{j\omega}{(j\omega + 1)(0.1j\omega + 1)}$$

- 12.21** Sketch the magnitude characteristic of the Bode plot for the transfer function

$$\mathbf{H}(j\omega) = \frac{10(5j\omega + 1)}{(100j\omega + 1)(0.02j\omega + 1)}$$

- 12.22** Sketch the magnitude characteristic of the Bode plot for the transfer function

$$\mathbf{H}(j\omega) = \frac{0.1(2j\omega + 1)}{j\omega(0.1j\omega + 1)(0.01j\omega + 1)}$$

- 12.23** Sketch the magnitude characteristic of the Bode plot for the transfer function

$$\mathbf{H}(j\omega) = \frac{0.5(10j\omega + 1)(j\omega + 1)}{j\omega(0.1j\omega + 1)(0.01j\omega + 1)^2}$$

- 12.30** Determine $\mathbf{H}(j\omega)$ from the magnitude characteristic of the Bode plot shown in Fig. P12.30.

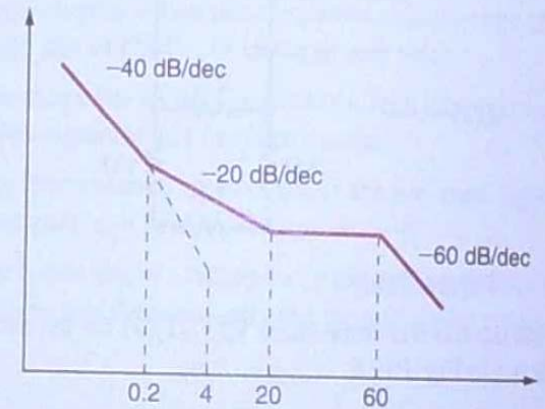


Figure P12.30

EEE 202 HW5 SOLUTIONS

12.43 $Z = 100 + 50 \times 10^{-3} j\omega + \frac{1}{5 \times 10^{-6} j\omega} = R + Ls + \frac{1}{Cs} \quad s = j\omega$

$I = \frac{V}{Z} = V \cdot \frac{s/L}{s^2 + R/Ls + 1/LC} \rightarrow \omega_0 = \sqrt{\frac{1}{LC}} = \underline{2000 \text{ rad/s}}$

$\zeta = \frac{R}{2} \sqrt{\frac{C}{L}} = \frac{1}{2}$

$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{2\zeta} = \underline{1}$

$BW = \frac{\omega_0}{Q} = \underline{2000 \text{ rad/s}}$

$P_{AV} = \frac{1}{2} |V_s| |I_s| \cos \theta$

$= \frac{|V_s|^2}{2} \cdot \frac{1}{|Z|} \cdot \cos(\angle Z)$

$= \frac{72}{|Z|} \cdot \cos(\angle Z) \quad ; \quad \text{At Resonance, } \omega = \omega_0 \text{ the magnitude}$

and phase expressions are $|\frac{1}{Z}| = \frac{\omega_0/L}{[(\frac{1}{LC} - \omega_0^2)^2 + (\frac{R}{L}\omega_0)^2]}^{1/2} = \frac{1}{R}$

$\angle Z = 90 - \tan^{-1}(\frac{R/L}{0}) = 0^\circ. \quad (\text{At resonance, } \frac{1}{Z} = \frac{1}{R}, \text{ real, positive})$

$\Rightarrow P_{AV} = \frac{72}{100} = \underline{0.72 \text{ (W)}}$


12.44 $I = \frac{V}{Z} = V \cdot \frac{s/L}{s^2 + R/Ls + 1/LC}$

$|I(\omega_0)| = 12$
 $\omega_0 = \frac{1}{\sqrt{LC}} = 1 \times 10^3 \quad \Rightarrow \underline{C = 0.1 \times 10^{-3} \text{ (F)}}$
 $L = 10 \times 10^{-3}$

$|I(\omega_0)| = 36 \frac{\frac{1}{\sqrt{LC}} \cdot \frac{1}{L}}{[(\frac{1}{LC} - \frac{1}{LC})^2 + R^2/L^2 \frac{1}{LC}]^{1/2}} = \frac{36}{R} = 12 \Rightarrow \underline{R = 3 \Omega}$

$\therefore Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \underline{\frac{10}{3}}, \quad BW = \frac{\omega_0}{Q} = \underline{300 \text{ rad/s}}$

12.8

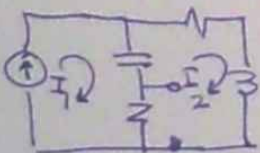

$I_1 = I_s$

$(I_2 - I_1)(4 + \frac{1}{s}) + I_2(2 + 2s) = 0$

$\Rightarrow I_2 = I_s \frac{4 + 1/s}{6 + 2s + 1/s} = I_s \frac{4s + 1}{2s^2 + 6s + 1}$


$V_o = (I_1 - I_2)4 = I_s \frac{8s^2 + 8s + 4}{2s^2 + 6s + 1}$

CORNER FREQUENCIES


BODE PLOT

12.9 $\frac{4j\omega+1}{20j\omega+1}$


zero $\frac{1}{4}$
pole $\frac{1}{20}$

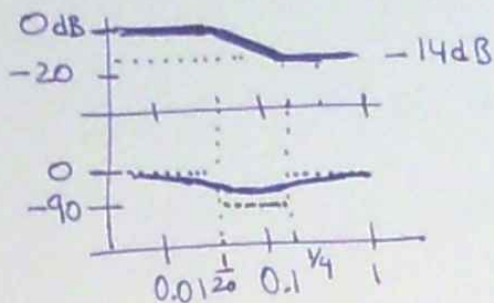

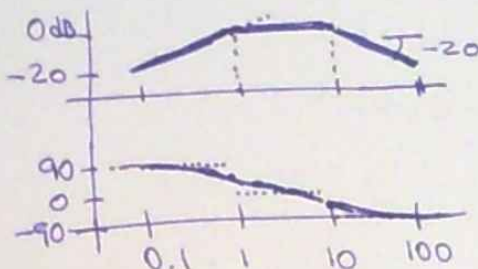
12.10 $\frac{j\omega}{(j\omega+1)(0.1j\omega+1)}$ zero 0 (0dB @ 1)
pole 1, 10



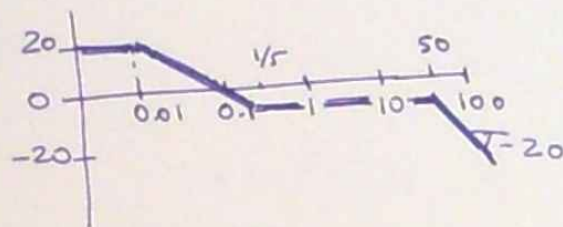
12.21 $\frac{10(5j\omega+1)}{(100j\omega+1)(0.02j\omega+1)}$ zero $\frac{1}{5}$
pole $\frac{1}{100}, 50$



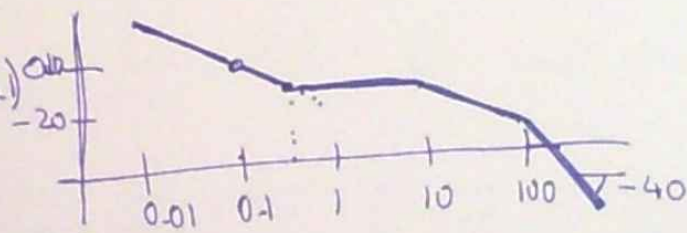12.22 $\frac{0.1(2j\omega+1)}{j\omega(0.1j\omega+1)(0.01j\omega+1)}$ zero: $\frac{1}{2}$
pole: 0 (0dB @ 0.1), 10, 100



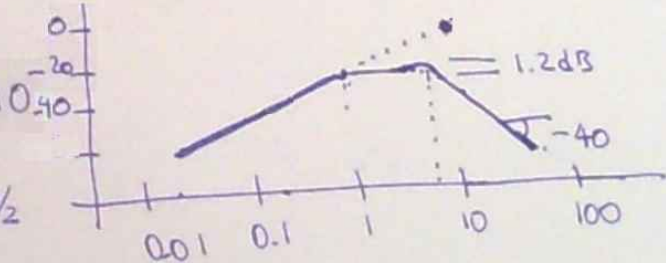12.26 $\frac{6.4j\omega}{(j\omega+1)(-w^2+8j\omega+4)}$ zero 0 (0dB @ 10)
pole 1, $\omega_0=8, \zeta=\frac{1}{2}$



12.27 Corner frequencies: zero: 0.1, 120
pole: 10, 80 (x2)
DC gain: 40dB (100)

- No phase information
⇒ assume minimum phase
i.e., all poles, zeros in left half plane.
- Cannot distinguish resonance
⇒ assume $\zeta=1$

$\therefore H(s) = 100 \frac{(\frac{1}{0.1}s+1)(\frac{1}{120}s+1)}{(\frac{1}{10}s+1)(\frac{1}{80}s+1)^2}$ ($s=j\omega$)

12.30 $H(s) = \frac{4}{j\omega} \frac{(\frac{1}{0.2}s+1)(\frac{1}{20}s+1)}{(\frac{1}{60}s+1)^3}$

zero: 0.2, 20
pole 0 (x2) 0dB @ 4
60 (x3)

14.6 Use Laplace transforms and nodal analysis to find $i_1(t)$ for $t > 0$ in the network shown in Fig. P14.6. Assume zero initial conditions.

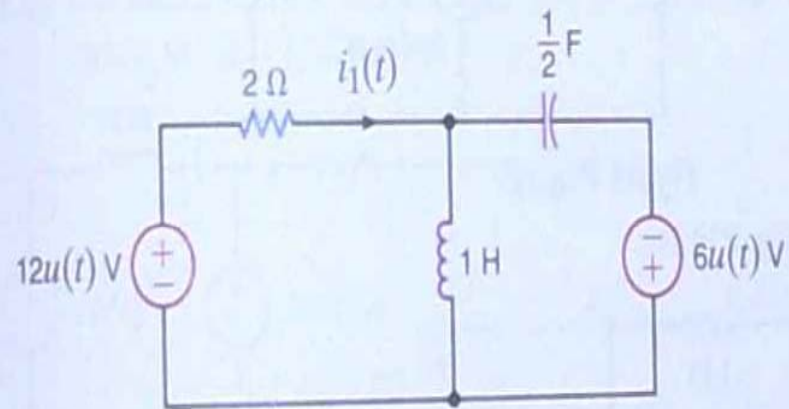


Figure P14.6

14.7 Use Laplace transforms to find $v(t)$ for $t > 0$ in the network shown in Fig. P14.7. Assume zero initial conditions.

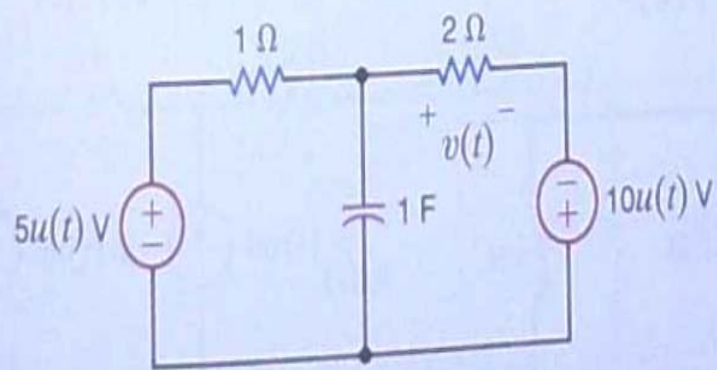


Figure P14.7

14.11 Find $v_o(t)$, $t > 0$, in the network shown in Fig. P14.11 using nodal analysis.

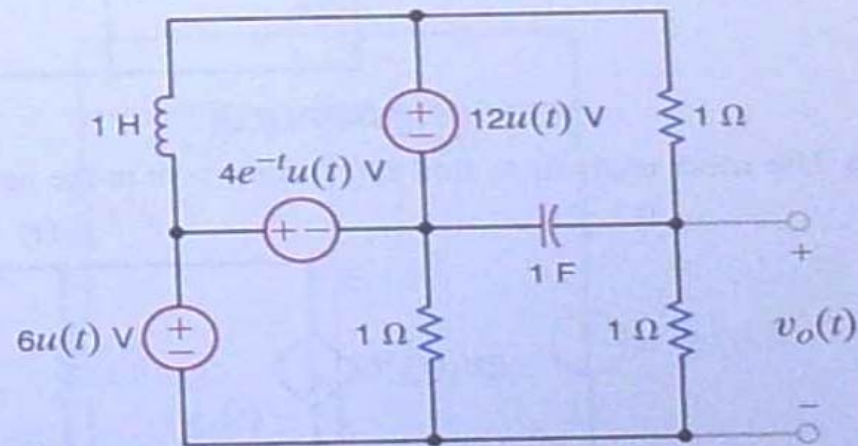


Figure P14.11

12.85 Given the second-order low-pass filter in Fig. P12.85, design a filter that has $H_o = 100$ and $f_c = 5$ kHz. Set $R_1 = R_3 = 1$ k Ω , and let $R_2 = R_4$ and $C_1 = C_2$. Use an op-amp model with $R_i = \infty$, $R_o = 0$, and $A = (2)10^5$.


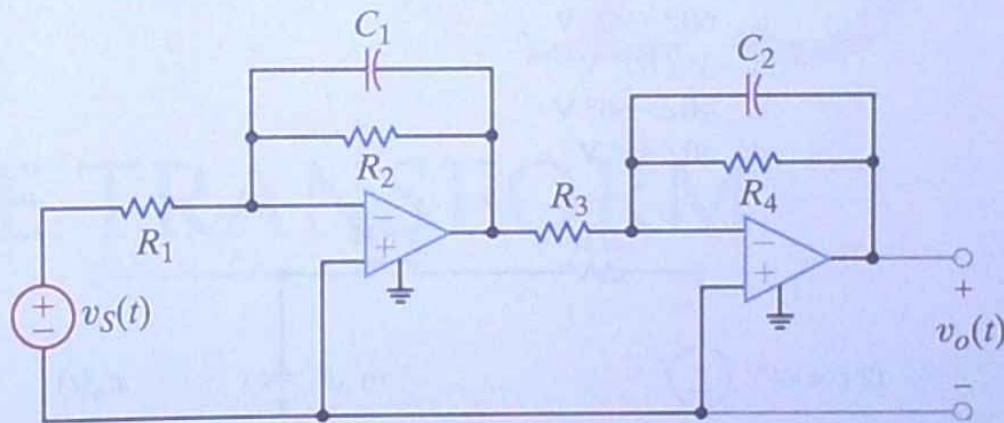


Figure P12.85

EEE 202 HW 6 SOLUTIONS

Pr. 14.6

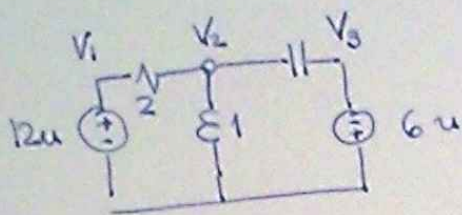

$$i_1(t) = \frac{V_1 - V_2(t)}{2} = \frac{12}{2} u(t) - \frac{V_2(t)}{2}$$

Node 1: $V_1 = 12 \cdot \frac{1}{s}$

Node 2: $\frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{1/Cs} + \frac{V_2}{1s} = 0$

$$\Rightarrow \frac{V_2 - V_1}{2} + \frac{1}{2s}(V_2 - V_3) + \frac{V_2}{1s} = 0$$

Node 3: $V_3 = -6 \cdot \frac{1}{s}$

Combining

$$\frac{1}{2}V_2 + \frac{1}{2}sV_2 + \frac{1}{s}V_2 = \frac{6}{s} + (-3\frac{s}{s})$$

$$\Rightarrow \left(\frac{1}{2}s^2 + \frac{1}{2}s + 1\right)V_2 = 6 - 3s \Rightarrow V_2(s) = \frac{(-3s + 6)^2}{s^2 + s + 2}$$

① Converting to table format: $\frac{*}{(s+a)^2 + b^2} = \frac{*}{s^2 + 2as + a^2 + b^2} \Rightarrow a = 1/2, b = \frac{\sqrt{7}}{2}$

$$V_2(s) = A \frac{s + 1/2}{(s + 1/2)^2 + 7/4} + B \frac{\sqrt{7}/2}{(s + 1/2)^2 + 7/4} \Rightarrow \begin{aligned} As + B\sqrt{7}/2 + A/2 &= -6s + 12 \\ \Rightarrow A &= -6 \\ B &= (12 + 3) \cdot \frac{2}{\sqrt{7}} \end{aligned}$$

$$V_2(t) = -6 \cdot e^{-1/2t} \cos \frac{\sqrt{7}}{2}t + \frac{30}{\sqrt{7}} \cdot e^{-1/2t} \sin \frac{\sqrt{7}}{2}t \quad t \geq 0$$

$$\Rightarrow i_1(t) = 6 - \left[\frac{15}{\sqrt{7}} \sin \frac{\sqrt{7}}{2}t - 3 \cos \frac{\sqrt{7}}{2}t \right] e^{-1/2t} \quad t \geq 0$$

② Alternative Soln.: Finding the PFE of $V_2(s) = \frac{-3 - 5.67j}{s + 0.5 - 1.32j} + \frac{(*)}{s + (*)}$

$$\Rightarrow V_2(s) = (-3 - 5.67j)e^{(-0.5 + 1.32j)t} + (*)$$

complex conjug of 1st term

$$= 2 \operatorname{Re} \left[(-3 - 5.67j)(e^{1.32jt}) e^{-1/2t} \right]$$

$$= 2 \operatorname{Re} \left[(-3 - 5.67j)(\cos 1.32t + j \sin 1.32t) \right] e^{-1/2t}$$

$$= 2 \left[-3 \cos 1.32t + 5.67 \sin 1.32t \right] e^{-1/2t}$$

etc

Pr 14.7

$$v(t) = v_2(t) - v_3(t) \quad \& \quad v(s) = v_2(s) - v_3(s)$$

$$v_1 = 5 \cdot \frac{1}{s}$$

$$v_3 = -10 \frac{1}{s}$$

$$\frac{v_2 - v_1}{1} + \frac{v_2 - v_3}{2} + \frac{v_2}{(1/1s)} = 0$$


$$\Rightarrow v_2 + \frac{1}{2}v_2 + s v_2 = v_1 + \frac{1}{2}v_3$$

$$(s + \frac{3}{2})v_2 = 0$$

$$\Rightarrow v_2(s) = 0 \Rightarrow v_2(t) = 0$$

$$\therefore v(t) = -v_3(t) = 10 u(t)$$

Pr 14.11

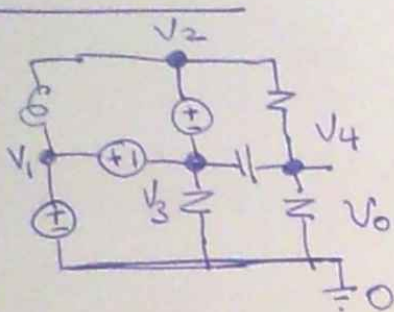

$$v_1 = \frac{6}{s}$$

$$v_1 - v_3 = \frac{4}{s+1} \Rightarrow v_3 = \frac{6}{s} - \frac{4}{s+1}$$

$$v_2 - v_3 = \frac{12}{s} \Rightarrow v_2 = \frac{18}{s} - \frac{4}{s+1}$$

$$\frac{v_4 - v_2}{1} + \frac{v_4 - v_3}{1/s} + \frac{v_4 - 0}{1} = 0$$

$$v_0 = v_4$$

$$\Rightarrow (s+2)v_4 = v_2 + v_3$$

$$\Rightarrow v_0 = \frac{1}{s+2} \cdot \left[\frac{24}{s} - \frac{8}{s+1} \right]$$

$$= \frac{24}{s(s+2)} - \frac{8}{(s+1)(s+2)} \stackrel{\text{PFE}}{=} \frac{12}{s} + \frac{-12}{s+2} + \frac{-8}{s+1} + \frac{8}{s+2}$$

$$\Rightarrow v_0(t) = 12u(t) - 4e^{-2t}u(t) - 8e^{-t}u(t)$$

$$\text{or } 12 - 4e^{-2t} - 8e^{-t} \quad t \geq 0.$$

Pr. 12.85 Try the ideal opamp case first: Each stage has transfer function

$$H_i(s) = -\frac{z_0}{R_i} = -\frac{R/RCs+1}{1k} \Rightarrow \text{Total t.f. } H(s) = H_i(s)H_i(s) = \frac{(R/1k)^2}{(RCs+1)^2}$$

- For $H_0 = 100$, $H(0) = 100 \Rightarrow \frac{R}{1k} = 10 \Rightarrow \underline{R = 10k.}$

- For $f_c = 5kHz \hat{=} 31.4k \text{ (rad/s)}$, an approximate solution would be to set the corner frequency ω_c equal to ω_c . That would produce a -6dB drop at f_c instead of -3dB because the filter is 2nd order.

Instead, we can solve $|H(j\omega_c)| = |H(0)|/\sqrt{2}$

$$\therefore \frac{(R/1k)^2}{(RQ\omega_c^2 + 1)} = \frac{(R/1k)^2}{\sqrt{2}} \Rightarrow (RC)^2 = \frac{\sqrt{2}-1}{\omega_c^2} \Rightarrow C = \frac{1}{10k \cdot 31.4k} \sqrt{\sqrt{2}-1}$$

$$= 2.05 \text{ nF.}$$

Computing the Bode plot in Matlab we verify that $H(s)$ has the desired properties $H(0) = 40 \text{ dB}$, $|H(j\omega)| = (40-3) \text{ dB}$ at 5 kHz .

Next, we analyze the effect of a non-ideal op-amp gain, $A = 2 \times 10^5$

The opamp equations become $V_o = A \cdot (V_- - 0)$

$$\frac{V_o - V_-}{z} + \frac{V_i - V_-}{R} = 0$$

Substituting, $V_o = -\frac{z}{1k} V_i \left[\frac{1}{\frac{A-1}{A} - \frac{z}{A \cdot 1k}} \right]$ for each stage

$$T(s)$$

Then, the total T.f. is $V_o = \left(-\frac{z}{1k}\right)^2 T^2 \cdot V_s = H(s) T(s)^2 V_s$

The deviation of T^2 from one determines the deviation of the transfer function H from the spec. Forming the Bode plot of $1-T^2$ (e.g. bode $(1-T^2)$) we find that it is smaller than -60 dB at all frequencies so the approximate solution is fairly accurate. Any further correction of the R,C values should be justified against the precision of their values.
