

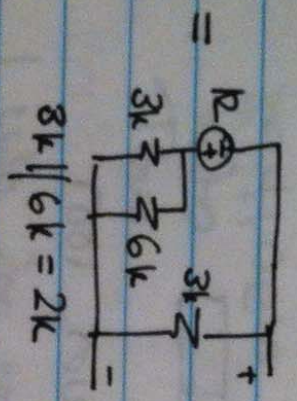


EEF 202 Hw 2 SOLUTIONS

S.23 1) $I_S = 0$



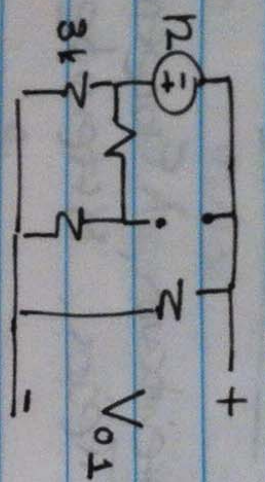


$8k \parallel 6k = 2k$

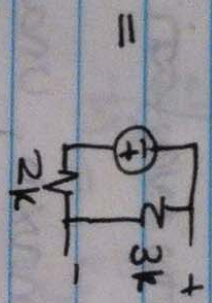


Voltage divider
 $V_{01} = -\frac{3k}{5k} \cdot 12$
 $= -\frac{36}{5} \text{ (V)}$

2) $V_S = 0$

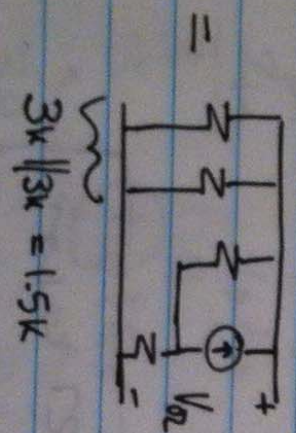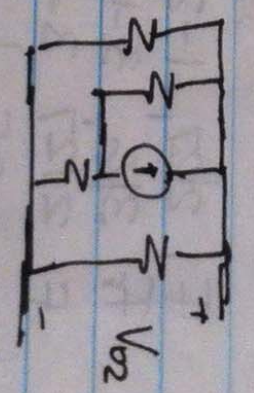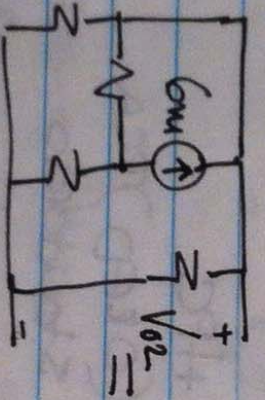


$3k \parallel 3k = 1.5k$

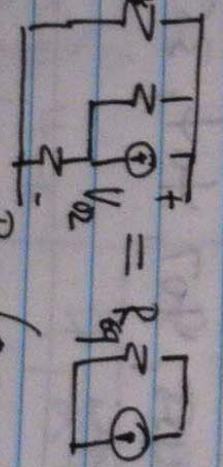

$R_{eq} = (1.5k + 3k) \parallel 3k$
 $= \frac{4.5k}{5}$

$\Rightarrow V_S = I_S R_{eq} = 6m \cdot \frac{9}{5}k = \frac{54}{5} \text{ (V)}$ voltage across \uparrow
 \Rightarrow Voltage drop across lower $3k$: $\frac{54}{5} \cdot \frac{3k}{3k + 1.5k} = \frac{36}{5} \text{ (V)}$


\therefore We have

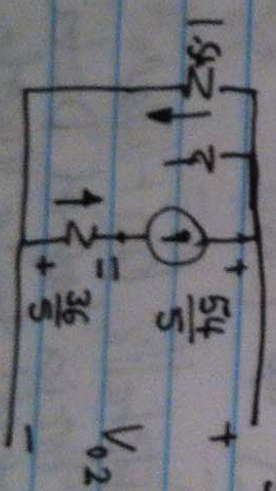


KVL: $-V_{02} + \frac{54}{5} - \frac{36}{5} = 0 \Rightarrow V_{02} = 18/5 \text{ (V)}$

$\Rightarrow V_0 = V_{01} + V_{02} = -\frac{36}{5} + 18/5 = -18/5 = -3.6 \text{ (V)}$

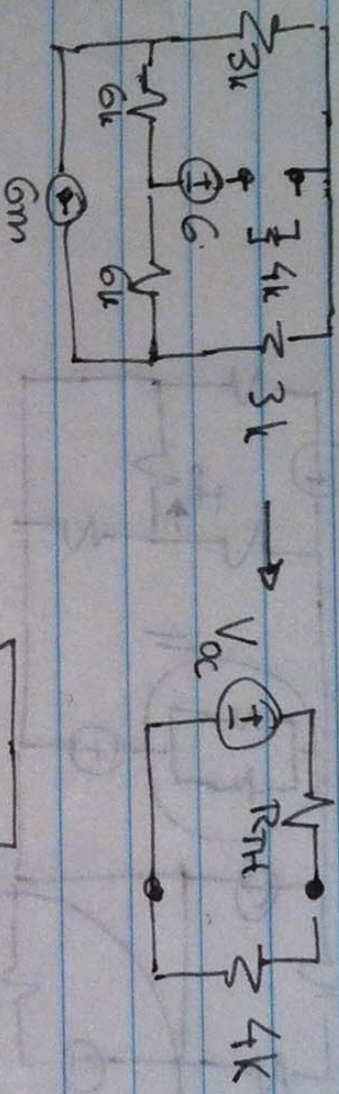5.35. To apply Thevenin, remove the "load" resistor and find V_{oc} and R_{TH} .



1). V_{oc} : Two loop current

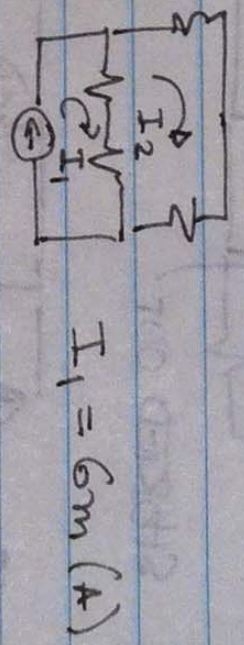


$$I_2(3k + 3k) + (I_2 - I_1)(6k + 6k) = 0 \Rightarrow I_2 = 4I_1(A)$$

$$KVL: -V_{oc} - 6 + I_2(3k) + (I_2 - I_1)6k$$

$$\Rightarrow V_{oc} = -6 + 12 + (-2)6 = \underline{\underline{-6(V)}}$$

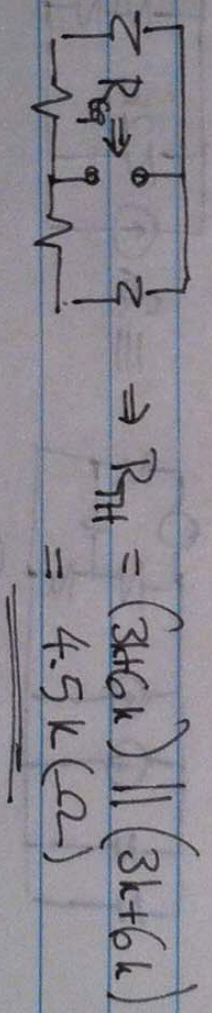
2). R_{TH} . Replace V_s by short, I_s by open.







\therefore Voltage division on equivalent circuit:

$$V_o = V_{oc} \cdot \frac{4k}{R_{TH} + 4k} = (-6) \frac{4k}{4.5k + 4k} = -\frac{48}{17} = \underline{\underline{-2.82(V)}}$$

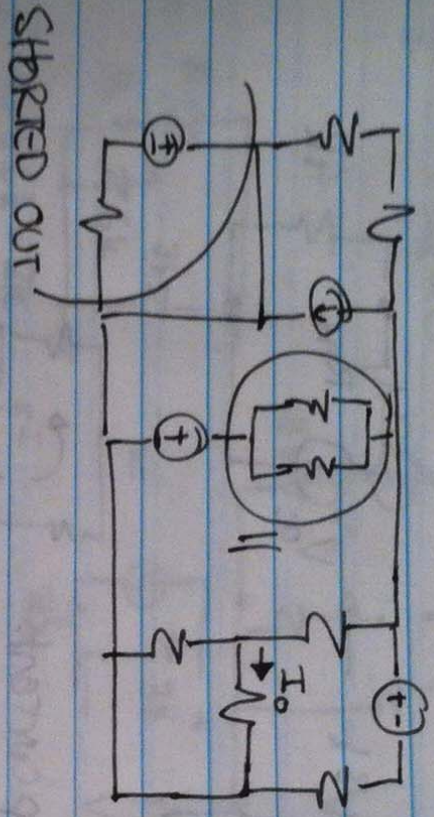5.95 Keep applying source transformations and element reduction steps:



SHORTED OUT

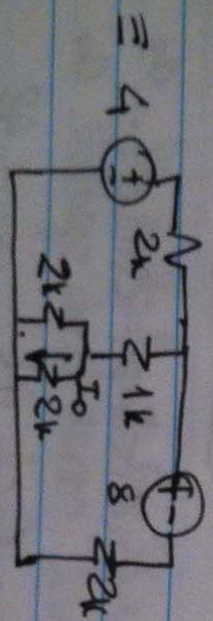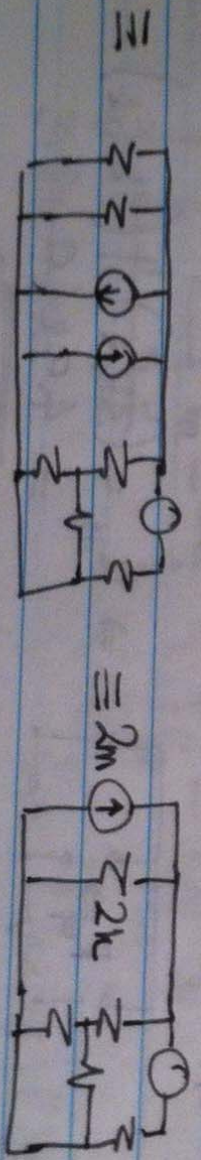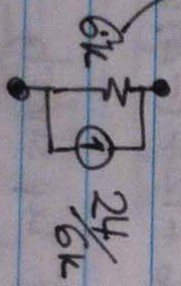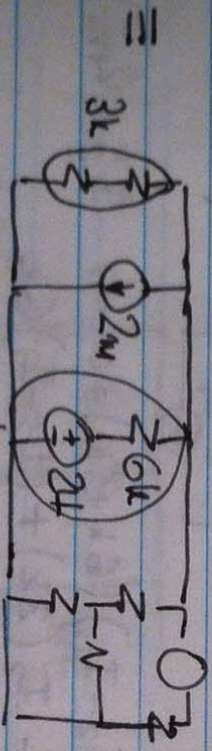

At this point we need to reduce the 2k resistors so the

Information on I_o will be lost and must be recovered later. Probably the easiest approach here is a loop analysis to compute the total current through the middle branch.

$$-4 + 2kI_1 + (I_1 - I_2)(1k + 1k) = 0$$

$$8 + 2kI_2 + (I_2 - I_1)(1k + 1k) = 0$$

$$I_o = \frac{1}{2}(I_1 - I_2)$$

$$\Rightarrow \boxed{I_o = 1 \text{ mA (A)}}$$