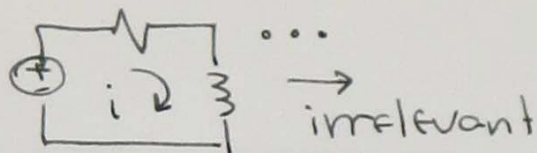


FEE 202 HW 3 SOLUTIONS

6.46 $E = \frac{1}{2} Li^2$


At ss, the inductor acts as a short so the effective circuit is



Then, $i = \frac{20}{1k} = 20 \text{ mA}$

$\rightarrow E = \frac{1}{2} 200 \text{ mH} \cdot (20 \text{ mA})^2 = 40 \mu\text{J}$

7.30 $t < 0$

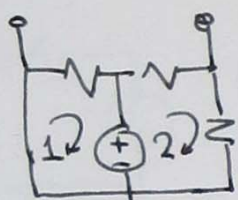


$6k I_1 + 6 = 0$

$6k I_2 + 6k I_2 - 6 = 0$

$\Rightarrow \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} -1 \text{ m} \\ 1/2 \text{ m} \end{pmatrix} \text{ A}$

KVL: $V_C(0^-) = -(\frac{1}{2} \text{ m} \cdot 6k - 1 \text{ m} \cdot 6k) = 3 \text{ V}$

$t > 0^+$

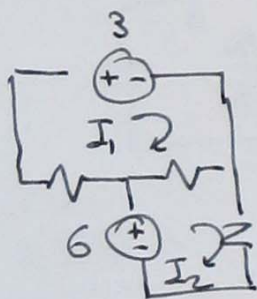


$3 + (I_1 - I_2)6k + I_1 6k = 0$

$(I_2 - I_1)6k + I_2 6k - 6 = 0$

$\Rightarrow \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} 0 \\ 1/2 \text{ m} \end{pmatrix} \text{ A}$

$\Rightarrow i_o(0^+) = I_2 - I_1(0^+) = \underline{\underline{1/2 \text{ mA}}}$ (IC)

$t > 0 (\rightarrow \infty)$

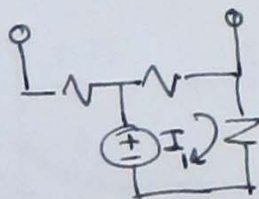


$i_o(\infty) = \frac{6}{12k} = 1/2 \text{ mA}$

$\Rightarrow i_o(t) = 1/2 \text{ mA}$, constant

For the computation of the time constant $\tau = \frac{RC}{R_{TH}}$, where


R_{TH} :

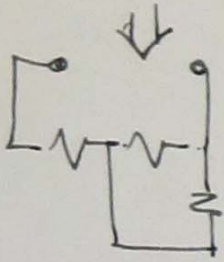

$$= 6k + (6k \parallel 6k) = 9k$$

$$\Rightarrow \tau = 0.45 \text{ s.}$$

7.60 $t < 0$

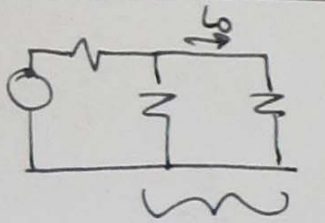


$$2 \parallel 2 = 1$$

i_0 is also the inductor current so it is continuous across $t = 0$.

By symmetry, $i_0(0^-) = \frac{1}{2} \left(\frac{-30}{5+1} \right)$

$$= \underline{\underline{-2.5 \text{ A.}}}$$


$t > 0$

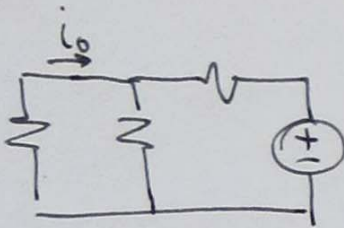

Again, by symmetry, $i_0 = -\frac{1}{2} i_s$

$$= -\frac{1}{2} \left(\frac{30}{2+1} \right) = \underline{\underline{-5 \text{ A.}}}$$

$\tau = \frac{L}{R_{TH}}$, where

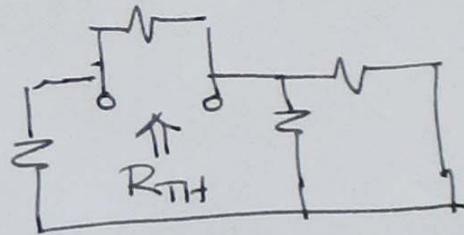

$$R_{TH} = 6 \parallel (2 + (2 \parallel 2))$$

$$= \underline{\underline{2 \Omega}}$$

$$\Rightarrow \tau = \frac{0.5}{2} = \underline{\underline{0.25 \text{ s.}}}$$

Collecting the various terms $(FV + (IC - FV)e^{-t/\tau})$

$$i_0(t) = -5 + (-2.5 + 5)e^{-t/0.25} \quad (\text{A})$$

