


$$8.51 \quad \textcircled{1} \quad \frac{12\angle 0 - V_1}{1} - 2\angle 0 - \frac{V_1}{1} + \frac{V_2 - V_1}{1} = 0$$

$$\textcircled{2} \quad \frac{V_1 - V_2}{1} - \frac{V_2}{-j} + 4\angle 0 = 0$$

$$\Rightarrow \begin{bmatrix} -1 & -1 & -1 \\ 1 & 1 & -1 \\ 1 & 1 & 1 \end{bmatrix} V = \begin{bmatrix} -12 + 2 \\ -4 \\ 4 \end{bmatrix} \Rightarrow V = \begin{bmatrix} 4.46 - 1.69j \\ 3.38 - 5.08j \end{bmatrix}$$

$$\Rightarrow I_o = \frac{V_1 - 0}{1} = 4.77 \angle -20.8^\circ \text{ (v)}$$

8.134

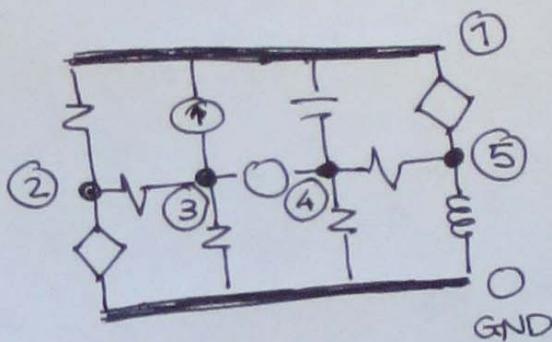

$$\textcircled{1} \quad \frac{V_2 - V_1}{1} + 2\angle 0 + \frac{V_4 - V_1}{-j} - 2I_x = 0 \quad \text{3} \quad I_x = \frac{V_4}{1}$$

$$V_x = V_3$$

$$\textcircled{2} \quad V_2 = 2V_x \quad \text{3}$$

$$\textcircled{3} \quad V_4 - V_3 = 12\angle 0$$

$$\textcircled{4} \quad \frac{V_1 - V_4}{-j} + \frac{V_5 - V_4}{1} + \frac{0 - V_4}{1} + \frac{0 - V_3}{1} + \frac{V_2 - V_3}{1} + -2\angle 0 = 0$$

$$\textcircled{5} \quad 2I_x + \frac{V_4 - V_5}{1} + \frac{0 - V_5}{j} = 0$$

$$I_o = \frac{V_2 - V_3}{1}$$

(supermode)

$$\left[ \begin{array}{c|c|c|c|c} -1+\frac{1}{j} & 1 & 0 & -\frac{1}{j}-2 & 0 \\ \hline 0 & 1 & -2 & 0 & 0 \\ \hline 0 & 0 & -1 & 1 & 0 \\ \hline -\frac{1}{j} & 1 & -1-1 & \frac{1}{j}-1-1 & 1 \\ \hline 0 & 0 & 0 & 2+1 & -1-\frac{1}{j} \end{array} \right] \quad V = \left[ \begin{array}{c} -2\angle 0 \\ \hline 0 \\ \hline 12\angle 0 \\ \hline 2\angle 0 \\ \hline 0 \end{array} \right]$$

$$I_o = [0, 1, -1, 0, 0] V = -13 - 12j$$

$$= 17.7 \angle -137^\circ \text{ (A)}$$

$$\begin{array}{|c|c|c|} \hline 1 & 2 & 3 \\ \hline 6 & 5 & 4 \\ \hline \end{array}$$

$$I_1 - I_2 = -2\angle 0$$

$$(I_2 - I_5)(-j) + 12\angle 0 + (I_1 - I_6)1 + I_1(1) = 0$$

$$I_x = I_5 - I_4$$

$$I_3 = 2I_x \quad 5$$

$$(I_4 - I_3)1 + I_4(j) + (I_4 - I_5)1 = 0$$

$$(I_5 - I_4)1 + (I_5 - I_6)1 - 12\angle 0 = 0$$

$$V_x = (I_6 - I_5)1$$

$$(I_6 - I_5)1 + (-2V_x) + (I_6 - I_1)1 = 0$$

$$I_o = I_6 - I_1$$

$$\left[ \begin{array}{c|c|c|c|c|c} 1 & -1 & 0 & 0 & 0 & 0 \\ \hline 1+j & -j & j & 0 & 0 & -1 \\ \hline 0 & 0 & 1 & 2 & -2 & 0 \\ \hline 0 & 0 & -1 & 1+j+1 & -1 & 0 \\ \hline 0 & 0 & 0 & -1 & 1+j & -1 \\ \hline -1 & 0 & 0 & 0 & -1+2 & 1-2+1 \end{array} \right] \quad I = \left[ \begin{array}{c} -2\angle 0 \\ -12\angle 0 \\ 0 \\ 0 \\ 12\angle 0 \\ 0 \end{array} \right]$$

$$I_0 = \left[ -1, 0, 0, 0, 0, 1 \right] I = -13 - 12j$$

$$= 17.7 \angle -137^\circ \text{ (A)}$$

$$\underline{8.135} \quad I_L = \frac{V_2}{j\omega L}, \quad I_C = \frac{\sqrt{2}}{(j\omega C)^{-1} + 150}$$

$$\text{For } |I_L| = |I_C|, \text{ we need } \left| \frac{1}{j\omega L} \right| = \left| \frac{1}{(j\omega C)^{-1} + 150} \right|$$

$$\Leftrightarrow \frac{1}{\omega L} = \frac{\omega C}{\sqrt{150^2 C^2 \omega^2 + 1}} \Leftrightarrow \left( \frac{1}{\omega L} \right)^2 = (\omega^2 C^2)^2$$

$$\Leftrightarrow \omega^4 L^2 C^2 - \omega^2 C^2 150^2 - 1 = 0$$

$$\Leftrightarrow \omega^4 - \omega^2 \frac{150^2}{L^2 C^2} - \frac{1}{L^2 C^2} = 0$$

Roots of quadratic  $2.254 \times 10^6, -4.44 \times 10^3$

$$\Rightarrow \omega^2 = 2.254 \times 10^6 \Rightarrow \omega = 1501.5 \text{ (rad/s)}$$