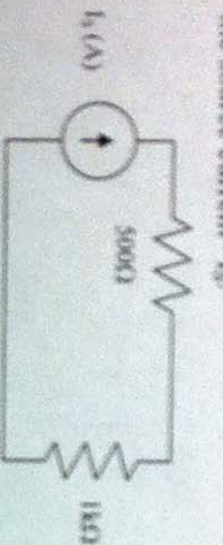


NAME: SOLUTIONS

ECE 202: Test 1

4 Problems, 30', Closed Book/Notes, 1 sheet of formulae allowed


Problem 1. In the following circuit, the 1k resistance absorbs 2W of power. Find the value of the source current " I_s ."



$$P = VI_s = RI_s^2 \Rightarrow 2 = 1k I_s^2$$


$$\Rightarrow I_s = \sqrt{0.002} = \underline{\underline{44.7 \text{ mA}}}$$

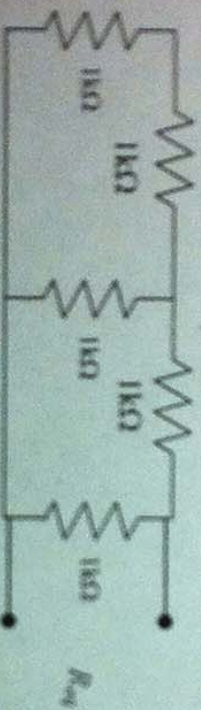Problem 2. Find the equivalent resistance of the following network.




$$R_{eq} = ((1k + 1k) \parallel 1k + 1k) \parallel 1k$$

$$= \frac{5}{8} k \Omega$$

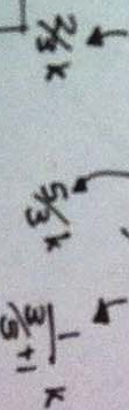


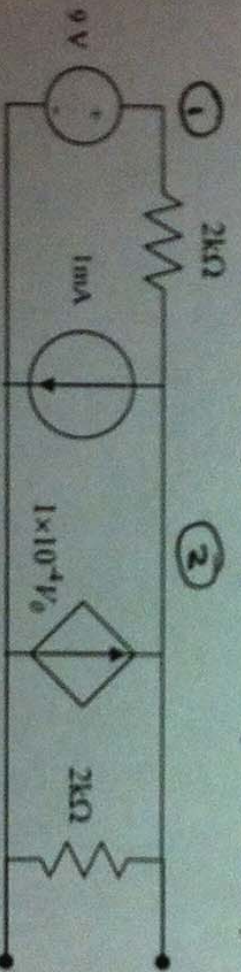Problem 3. Use Nodal analysis to write a set of equations to compute V_0 in the following circuit.



$$\begin{aligned} \bullet V_1 &= 9 \\ \bullet \frac{V_1 - V_2}{2k} - 1\text{mA} + 10^{-4} V_0 + \frac{0 - V_0}{2k} &= 0 \\ \bullet V_0 &= V_2 \end{aligned}$$

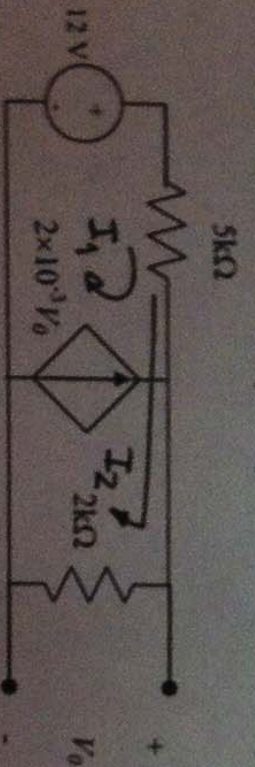Problem 4. Use Loop Analysis to write a set of equations to compute V_0 in the following circuit.



$$\begin{aligned} \bullet I_1 &= -2 \cdot 10^{-3} V_0 \\ \bullet -12 + (I_1 + I_2) 5k + I_2 2k &= 0 \\ \bullet V_0 &= I_2 2k \end{aligned}$$