


EEE 202, TEST 4

NAME: _____ SOLUTIONS _____

Closed-book/notes, 2 problems, equal credit, 1 sheet of formulae allowed

Problem 1: RC-filters are often used to reduce the effect of high-frequency noise or low-frequency drift in circuits. In the following example, the voltage source represents a mid-frequency useful signal (e.g., voice) that is to be transmitted to the output (V_{out}) with little change, while the DC component is eliminated.

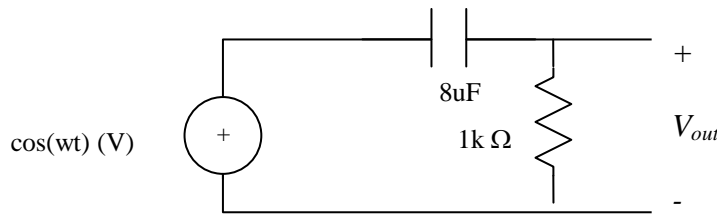1. Write an expression for the steady-state V_{out}
2. Show that DC is eliminated, i.e., $V_{out} = 0$ for $w = 0$, at steady-state.
3. What is the amplitude of V_{out} at $w = 40\text{Hz}$?




$$1. V_{out} = \frac{R}{R + \frac{1}{sC}} V_{in} = \frac{RCs}{RCs + 1} V_{in} \text{ with } s = jw, V_{in} = 1\angle 0^\circ,$$

$$V_{out} = \frac{RCw}{\sqrt{(RCw)^2 + 1}} \angle 90^\circ - \tan^{-1}(RCw)$$

2. From the expression above, the amplitude of V_{out} is 0 when $w = 0$.
3. At 40Hz, $w = 40 \times 2\pi = 251.3$. Evaluating the amplitude for $RC = 8\text{m}$, we find $|V_{out}| = 0.895$

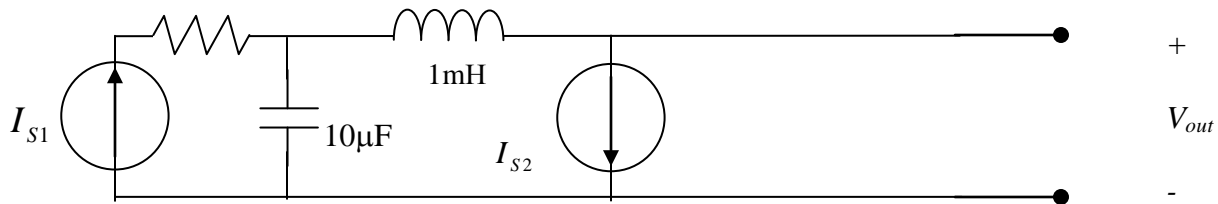Problem 2. In the following circuit, $I_{S1}(t) = 0.001 \cos(10t)$ (A), $I_{S2}(t) = 0.01 \cos(10t + 45^\circ)$ (A). Write a set of equations to compute the voltage V_{out} .



Nodal Analysis: 3 nodes, left-to-right V_1, V_2, V_3 , $V_{out} = V_3$:

$$\begin{aligned} 1. I_{S1} + \frac{V_2 - V_1}{R} &= 0, & 0.001\angle 0 + \frac{V_2 - V_1}{1k} &= 0 \\ 2. \frac{V_1 - V_2}{R} + \frac{0 - V_2}{\frac{1}{jwC}} + \frac{V_3 - V_2}{jwL} &= 0, & \frac{V_1 - V_2}{1k} - V_2 j100\mu + \frac{V_3 - V_2}{j10m} &= 0 \\ 3. -I_{S2} + \frac{V_3 - V_2}{jwL} &= 0, & -0.01\angle 45^\circ + \frac{V_3 - V_2}{j10m} &= 0 \end{aligned}$$

Loop Analysis: 2 loops, left-to-right I_1, I_2 (CW)

$$\begin{aligned} 1. I_1 = I_{S1}, I_2 = I_{S2}, & \left(\frac{1}{jwC}\right)(I_2 - I_1) + jwL(I_2) + V_{out} = 0, \\ & V_{out} = \left(\frac{1}{j100\mu}\right)(0.001\angle 0 - 0.01\angle 45^\circ) - j10m0.01\angle 45^\circ + \end{aligned}$$