
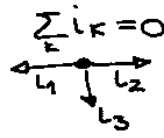



ECE 301 REVIEW NOTES

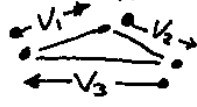
① Power (instantaneous) $P(t) = v(t) i(t)$
Ohm  , Kirchoff: KCL $\sum i_k = 0$



KVL $\sum V_k = 0$

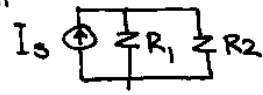
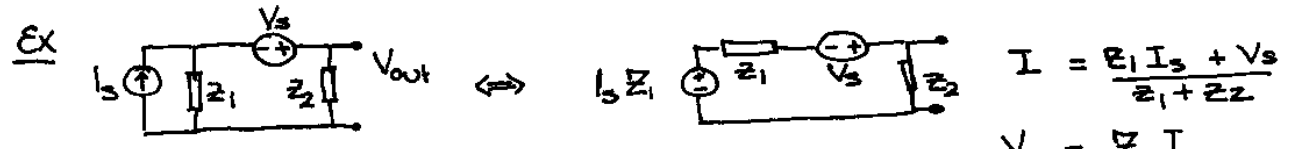
② Simple Circuits

• Single loop  $i = \frac{V_s}{R_1 + R_2}$; $V_{R_2} = \frac{R_2}{R_1 + R_2} V_s$
 - Max Power Transfer $\max_{R_2} P_{R_2} = \frac{V_s^2}{4R_1}$ @ $R_1 = R_2$

• Single node-pair  $V = \frac{I_s}{\frac{1}{R_1} + \frac{1}{R_2}}$; $I_{R_2} = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} I_s$

③ Steady-state Analysis

- DC: Capacitors \rightarrow Open, Inductors \rightarrow Short
- AC: $V = ZI$; $V = V_0 \cos(\omega t + \theta) = V_0 \angle \theta$ (phasor notation)
 $I = I_0 \cos(\omega t + \phi) = I_0 \angle \phi$
 $Z = |Z| e^{j\angle Z}$ Complex impedance
 $\rightarrow V_0 = |Z| I_0, \theta = \phi + \angle Z$
- Complex arithmetic: $a + jb = m e^{j\theta}$; $m = \sqrt{a^2 + b^2}$
 $\theta = \begin{cases} \tan^{-1}(b/a) & \text{if } a > 0 \\ \tan^{-1}(b/a) + \pi & \text{if } a < 0 \end{cases}$
- Impedances: Resistor $Z_R = R$, Capacitor $Z_C = \frac{1}{j\omega C}$
 Inductor $Z_L = j\omega L$
- With these definitions, solve circuits as usual (nodal, loop, superposi etc)




Computational details: Suppose $I_s = I_0 \angle \phi_I, V_s = V_0 \angle \phi_V$
 Then $V_{out} = \frac{Z_2 Z_1}{Z_1 + Z_2} I_s + \frac{Z_2}{Z_1 + Z_2} V_s = \frac{Z_2 Z_1}{Z_1 + Z_2} (I_0 e^{j\phi_I}) \angle 0 + \frac{Z_2}{Z_1 + Z_2} (V_0 e^{j\phi_V}) \angle 0$
 $= \left\{ \frac{R_1 Z_2}{Z_1 + Z_2} I_0 e^{j\phi_I} + \frac{Z_2}{Z_1 + Z_2} V_0 e^{j\phi_V} \right\} \angle 0$
 ← Complex arithmetic → ↔ time function

④ Circuit Analysis

- NODAL : - Define nodes 1...N and Voltages $V_1 \dots V_N$
 - Write KCL at each node in terms of Voltages
 - Final result $Ax = b$, $x =$ node voltages

Ex:

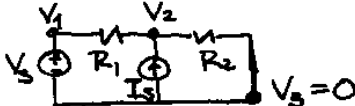


$$\left. \begin{aligned} V_1 &= V_s \\ \frac{V_2 - V_1}{R_1} + \frac{V_2 - V_0}{R_2} - I_s &= 0 \end{aligned} \right\} \Rightarrow \begin{bmatrix} 1 & 0 \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} \end{bmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} V_s \\ -I_s \end{pmatrix}$$

- Special cases: Some Voltage sources \rightarrow "Supernodes"
 Dependent sources \rightarrow Additional variables (and equations)


- LOOP/MESH: - Define loops 1...N and Currents $i_1 \dots i_N$
 - Write KVL for each loop in terms of currents
 - Final result $Ax = b$, $x =$ loop currents
 - Special cases: Current sources \rightarrow "supermesh"
 Dependent sources \rightarrow Additional variable

Ex

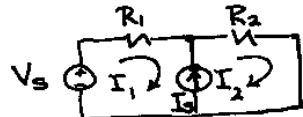

$$\left. \begin{aligned} I_1 - I_2 &= -I_s \\ -V_s + R_1 I_1 + R_2 I_2 &= 0 \end{aligned} \right\} \Rightarrow \begin{bmatrix} 1 & -1 \\ R_1 & R_2 \end{bmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} -I_s \\ V_s \end{pmatrix}$$

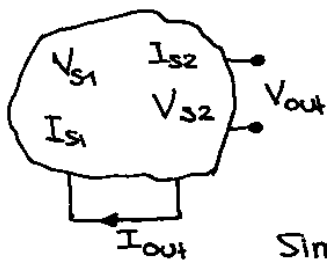- SUPERPOSITION: In circuits with multiple independent sources the voltages / currents depend linearly on the sources.




$$V_{out} = f(V_{s1}, V_{s2}, I_{s1}, I_{s2}) ; f = \text{Linear function}$$

$$\Rightarrow V_{out} = \alpha_1 V_{s1} + \alpha_2 V_{s2} + \alpha_3 I_{s1} + \alpha_4 I_{s2} ; \alpha_i = \text{coefficient}$$


Similarly $I_{out} = \beta_1 V_{s1} + \beta_2 V_{s2} + \beta_3 I_{s1} + \beta_4 I_{s2}$.

- Solution Approach:
- Keep one source at a time, replace the rest with zero sources, compute V_{out} (or I_{out}), and add up all contributions.
 - Zero sources: Voltage \equiv short circuit
 Current \equiv open circuit
 - Do not replace dependent sources!
 (Keep them as they are in all partial computations)

Ex:

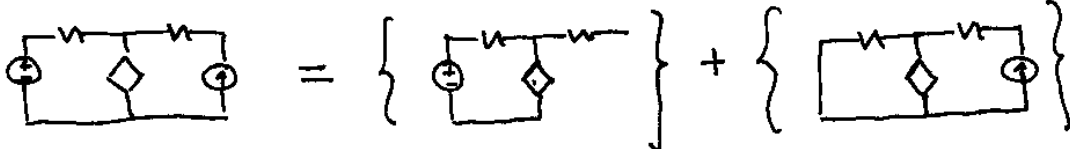

• SOURCE TRANSFORMATION

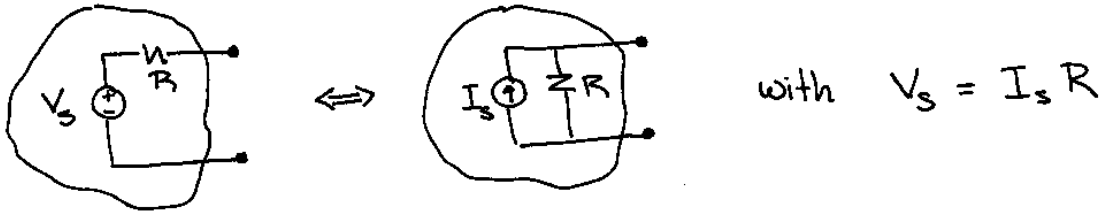

• THEVENIN - NORTON EQUIVALENTS

Two-terminal circuit



Computations:

- ① V_{oc} : $V_x = V_{oc}$
- ② I_{sc} : $I_x = I_{sc}$
- ③ $R_{TH} = \frac{V_{oc}}{I_{sc}}$ (in general)

Special Cases:

■ No dependent sources $R_{TH} = R_{eq} \rightarrow \begin{cases} V_{sk} = 0 \\ I_{sk} = 0 \end{cases}$

$V_{sk} = 0 \rightarrow$ Replace voltage sources with shorts


$I_{sk} = 0 \rightarrow$ Replace current sources with opens

■ No independent sources: Apply a test source. + compute R_{TH} .




Either current or voltage sources can be used unless the circuit is singular ($R_{TH} = 0$ or ∞); If so, one type of test source will yield R_{TH} and the other will result in inconsistent equations.

⑤ Op - Amps

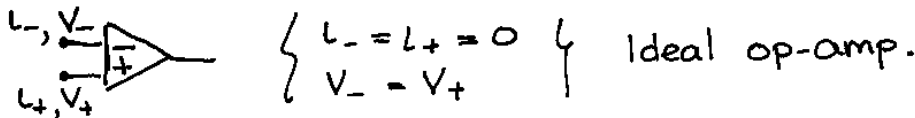

3 basic configurations

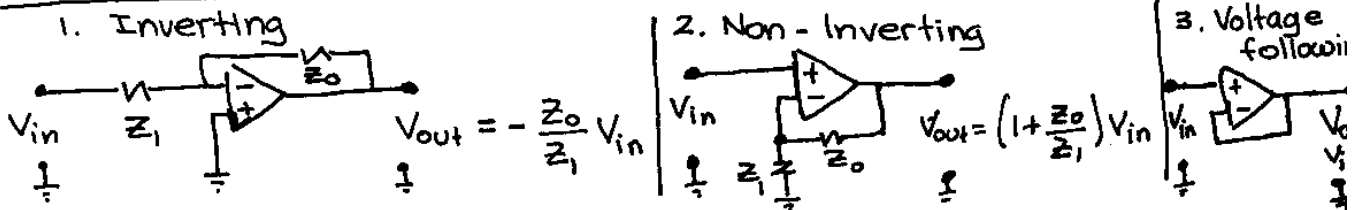

⑥ Energy Storage Elements (Capacitors - Inductors) -4/5-

Capacitors: $i_c = C \frac{dV_c}{dt} \Rightarrow V_c(t) = V_c(0) + \frac{1}{C} \int_0^t i_c(\tau) d\tau$



Energy stored: $W_c = \int v i = \frac{C V_c^2(t)}{2}$

Inductors: $v_L = L \frac{di_L}{dt} \Rightarrow i_L(t) = i_L(0) + \frac{1}{L} \int_0^t v_L(\tau) d\tau$


Energy stored: $W_L = \int v i = \frac{L i_L^2(t)}{2}$

6.1 1st Order Circuits

ODE (canonical form) $T \frac{dy}{dt} + y(t) = x(t)$. $T = \text{time-constant}$

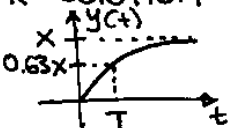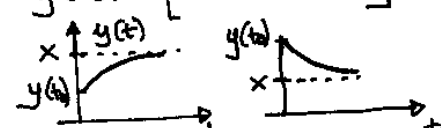
- Constant- x solution: $y(t) = e^{-\frac{t-t_0}{T}} y(t_0) + \left[1 - e^{-\frac{t-t_0}{T}}\right] x$
- If $y(t_0) = 0$  ; if $y(t_0) \neq 0$ 

• TYPICAL RC CIRCUIT

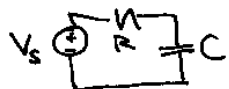

$RC \frac{dV_c}{dt} + V_c = V_s$; $T = RC$

• TYPICAL RL CIRCUIT

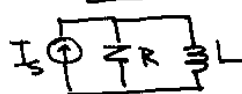

$\frac{L}{R} \frac{di_L}{dt} + i_L = I_s$; $T = \frac{L}{R}$


6.2 2nd Order Circuits

ODE (canonical form) $\frac{d^2 y}{dt^2} + 2\zeta\omega_0 \frac{dy}{dt} + \omega_0^2 y = x(t)$; $\zeta = \text{damping ratio}$

$\omega_0 = \text{natural undamped frequency}$.


- $\zeta < 1$ underdamped response
oscillation amplitude \uparrow as $\zeta \downarrow$
 $\omega_0 \sim \text{frequency of oscillation}$

$x = \text{const.}$

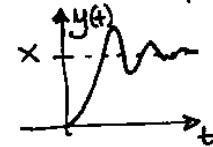



- $\zeta > 1$ overdamped response

$x = \text{const.}$

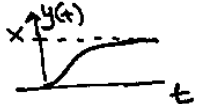

6.3 Circuits with switches (DC SOURCES)

(Transient Analysis)

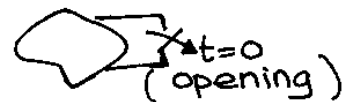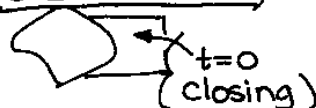


- KEY PRINCIPLE: Capacitor Voltages and Inductor Currents are continuous at the switching time.
e.g. $V_c(0^-) = V_c(0^+)$, $i_L(0^-) = i_L(0^+)$

• SOLUTION PROCEDURE:

- ① Compute the solution for the continuous variables
- ② Compute the solution for the variables of interest:

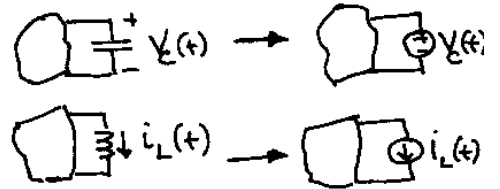- Replace the capacitors with time-dependent voltage sources and the inductors with time-dependent current sources, and then solve the resulting resistive circuit.



① Solution for the continuous variables.

- $t < 0$ steady-state \rightarrow Initial conditions for the $t > 0$ solution
- 1st order circuits: ODE has the form $T \frac{dy}{dt} + y(t) = y_\infty$; $y(0) = y_{0-}$
 where T is the circuit time-constant.
 y is the variable of interest (V_c or i_L)
 y_∞ is the $t > 0$ steady-state
 y_{0-} is the $t < 0$ steady-state

\Rightarrow SOLUTION PROCEDURE:

- 1.1 Compute the $t < 0$ steady-state to find y_{0-} .
 Capacitors \rightarrow open, Inductors \rightarrow short, switches @ $t < 0$ position:
 \rightarrow solve the resistive network for y .
- 1.2 Compute the $t > 0$ steady-state to find y_∞ .
 Capacitors \rightarrow open, Inductors \rightarrow short, switches @ $t > 0$ position:
 \rightarrow solve the resistive network for y .
- 1.3 Compute the Thevenin-equivalent resistance as seen from the capacitor/inductor terminals. Then find the circuit time constant as $T = R_{TH}C$ or $T = L/R_{TH}$
- 1.4 Form the solution for $y(t)$, $t > 0$: $y(t) = K_1 + K_2 e^{-t/T}$
 $K_1 = y_\infty$, $K_1 + K_2 = y_{0-}$

Note: singular cases where $R_{TH} = 0$ or ∞ may require special treatment.

