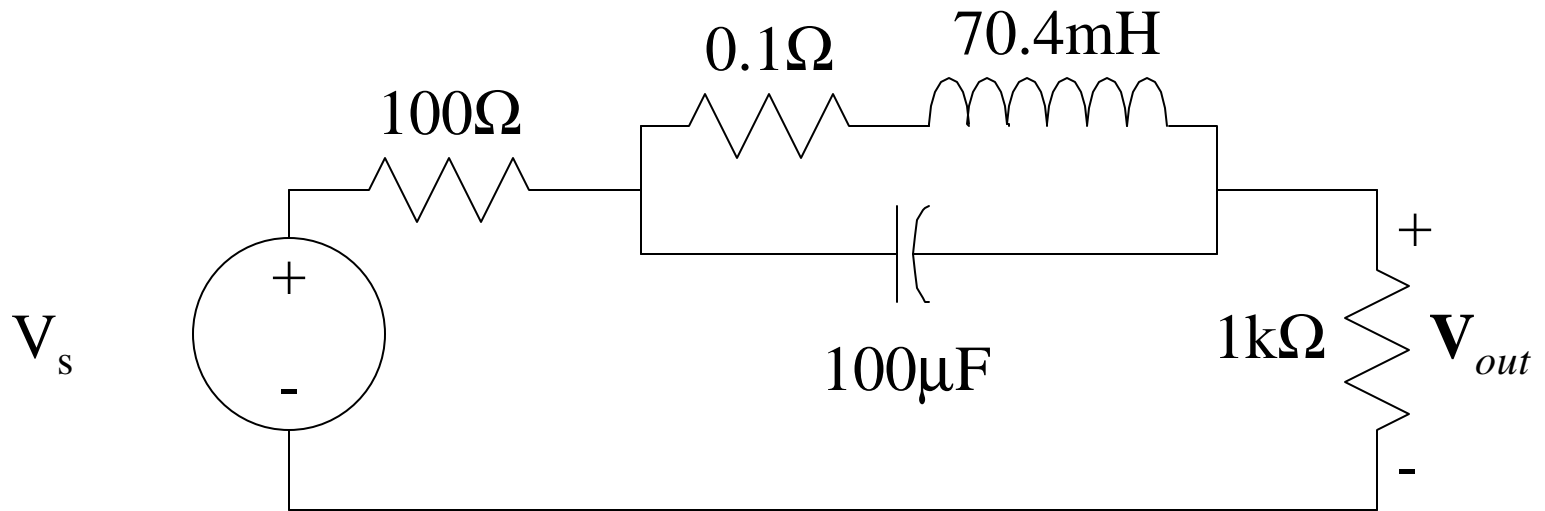


# Notch Filter Computations



$$V_s = ZI; \quad V_o = R_3 I = \frac{R_3}{Z} V_s$$

$$Z = R_1 + R_3 + Z_e; \quad Z_e = \left( \frac{1}{sL + R_2} + sC \right)^{-1} = \frac{sL + R_2}{s^2 LC + sCR_2 + 1}$$


$$Z = \frac{s^2 LC(R_1 + R_3) + s[CR_2(R_1 + R_3) + L] + (R_1 + R_2 + R_3)}{s^2 LC + sCR_2 + 1}$$

$$V_o = \frac{s^2 LCR_3 + sCR_2 R_3 + R_3}{s^2 LC(R_1 + R_3) + s[CR_2(R_1 + R_3) + L] + (R_1 + R_2 + R_3)} V_s$$
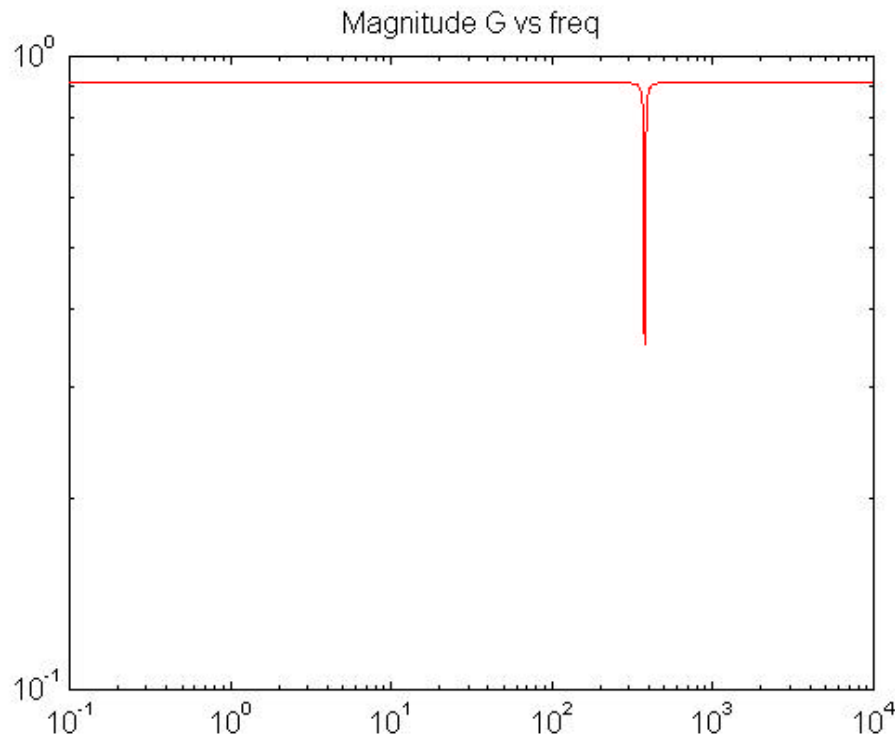
# Matlab Computations

Let's find the frequencies rejected by this filter using Matlab:

```
» L=70.4e-3;R1=100;R2=0.1;R3=1e3;C=100e-6;    % define the component values
» w=logspace(-1,4,1000); s=j*w ;                % define a frequency vector
» % compute the frequency response
» G=(s.*s*L*C*R3+s*C*R2*R3+R3)./(s.*s*L*C*(R1+R3)+s*(C*R2*(R1+R3)+L)+R1+R2+R3);
» loglog(w,abs(G))                             % and plot the magnitude
```





From the plot, this notch filter should attenuate frequencies  $\sim 370$ (rad/s)
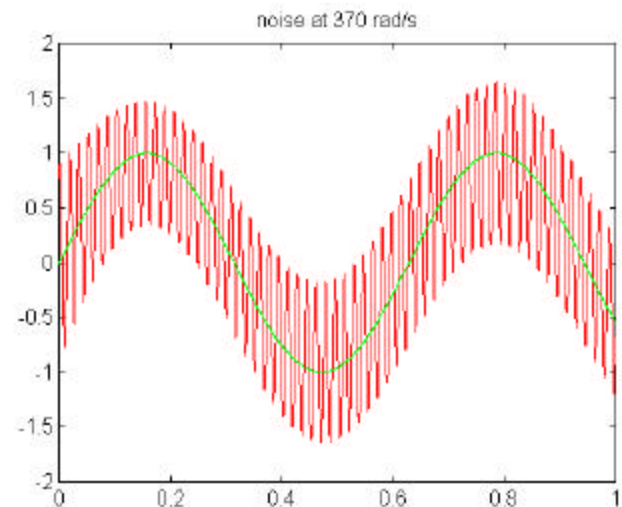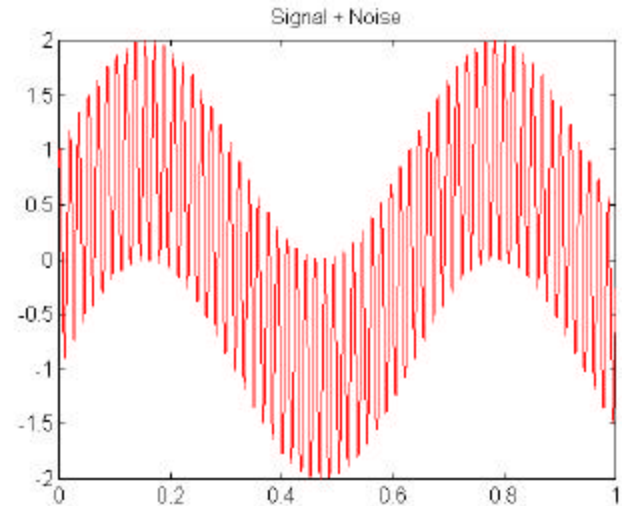
# Matlab Simulation

Now, let's visualize how this filter works:

```
» t=[0:1e-4:1]';           % Define a time vector
» V0=sin(10*t);            % and a "useful signal"
» noise=sin(370*t+1);      % which is corrupted by noise.
» Vs = V0+noise;           % This is what we measure
» plot(t,Vs)
»
»
» % Simulate the filter response and compare the result
» % with the original signal V0
» Vout=lsim([L*C*R3,C*R2*R3,R3],[L*C*(R1+R3),(C*R2*(R1+R3)+L),R1+R2+R3],Vs,t);
» plot(t,Vout,t,V0)
»
» % The result is only a little less noisy than Vs
```





NOTE: For a brief explanation and calling format of Matlab commands use "help", e.g., >> help lsim
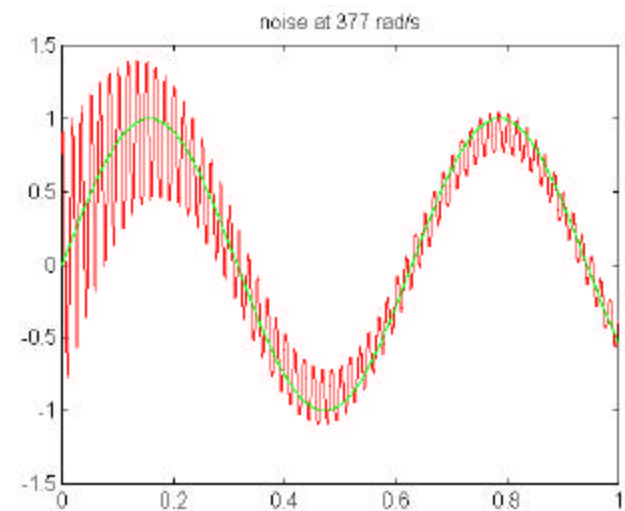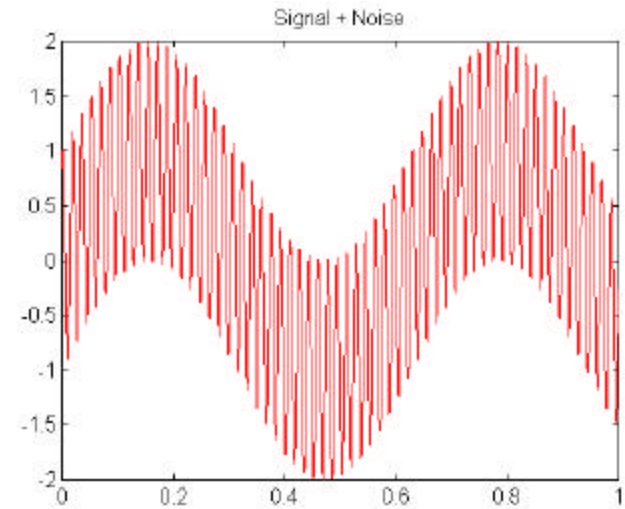
# Matlab Simulation

For a noise frequency 377 (rad/s):

```
» noise=sin(377*t+1);    % New noise.  
» Vs = V0+noise;        % This is what we measure  
» plot(t,Vs)  
»  
»  
»  
» % Simulate the filter response and compare the result  
» % with the original signal V0  
» Vout=lsim([L*C*R3,C*R2*R3,R3],[L*C*(R1+R3),(C*R2*(R1+R3)+L),R1+R2+R3],Vs,t);  
» plot(t,Vout,t,V0)  
»  
» % Impressive! The filter is very selective.
```



# Matlab Simulation

Finally, let's try to predict how much the noise is attenuated using AC analysis.

E.g, filtered noise =  $G(j370)$ \*input noise

We need to use the concept of linearity, that is filtered (signal+noise) = filtered(signal)+filtered(noise)

»  $s=j*10$

»  $G=(s.*s*L*C*R3+s*C*R2*R3+R3)./(s.*s*L*C*(R1+R3)+s*(C*R2*(R1+R3)+L)+R1+R2+R3)$

G =

0.9090 - 0.0006i

Use abs and angle to get the polar form:  $G(j10) = 0.909\angle 0.0006$

And for  $s = j*377$ , we get  $G = 0.1232 + 0.0170i$ :  $G(j377) = 0.124\angle 0.137$  (angles in rad)

So, in our phasor notation,

$$\begin{aligned}V_{out} &= G(j10)V_0 + G(j377)noise \\ &= [0.909\angle 0.0006][1\angle -1.57]_{|w=10} + [0.137\angle 0.124][1\angle -0.57]_{|w=377} \\ &= [0.909\angle -1.5694]_{|w=10} + [0.137\angle -0.446]_{|w=377}\end{aligned}$$

$$V_{out}(t) = 0.909\cos(10t - 1.57) + 0.137\cos(377t - 0.446)$$

The noise amplitude was reduced by a factor of 7, but in the process, 10% of the signal was lost too.

Notice that this expression is the steady-state voltage out, while in our previous simulation the plot includes the initial transient, lasting approximately 0.5 (s).