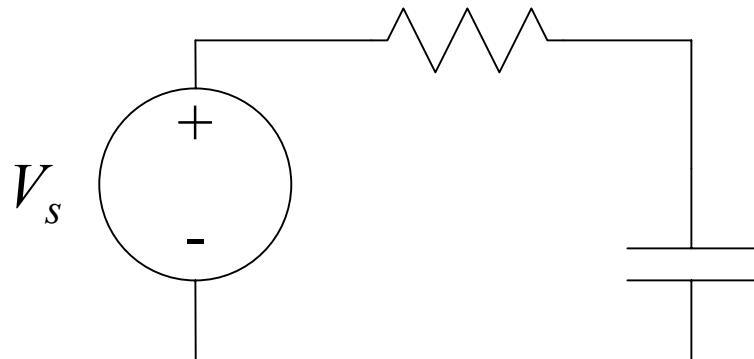


Solution of 1st-order linear ODEs

$$T \frac{dy}{dt}(t) + y(t) = x(t) \Rightarrow y(t) = e^{-\frac{t-t_0}{T}} y(t_0) + \frac{1}{T} \int_{t_0}^t e^{-\frac{t-\tau}{T}} x(\tau) d\tau$$

$$x(t) = x = \text{const.} \Rightarrow y(t) = e^{-\frac{t-t_0}{T}} y(t_0) + \left[1 - e^{-\frac{t-t_0}{T}} \right] x = x - e^{-\frac{t-t_0}{T}} [x - y(t_0)]$$

Solutions of Simple RC Circuits




$$v_c + Ri = V_s; \quad i = C \frac{dv_c}{dt} \Rightarrow$$

$$RC \frac{dv_c}{dt} + v_c = V_s \Rightarrow$$

$$v_c(t) = e^{-\frac{t}{RC}} v_c(0) + \frac{1}{RC} \int_0^t e^{-\frac{t-\tau}{RC}} V_s(\tau) d\tau$$

$$\text{const.} V_s, \quad v_c(t) \rightarrow V_s$$


Solutions of Simple RC Circuits (cont.)

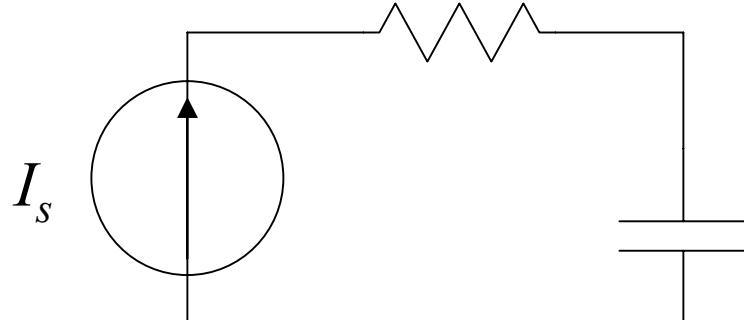

$$v_R = RI_s; \quad I_s = C \frac{dv_c}{dt} \Rightarrow$$


$$v_c(t) = v_c(0) + \frac{1}{C} \int_0^t I_s(\tau) d\tau$$
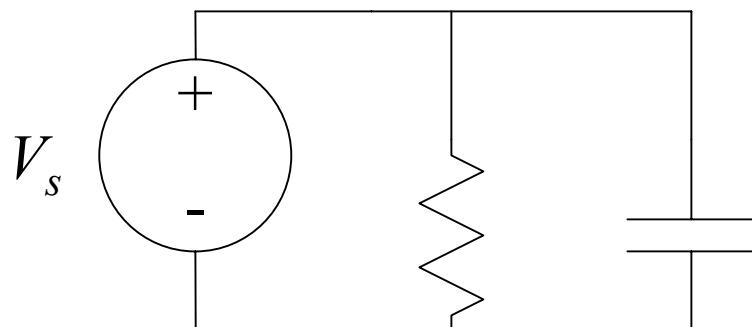
$$\text{const. } I_s, \quad v_c(t) = v_c(0) + \frac{I_s}{C} t \rightarrow \infty$$



$$v_R = v_c = V_s; \quad i_c = C \frac{dV_s}{dt} \Rightarrow$$

discont. V_s , $i_c(t)$ not well-defined

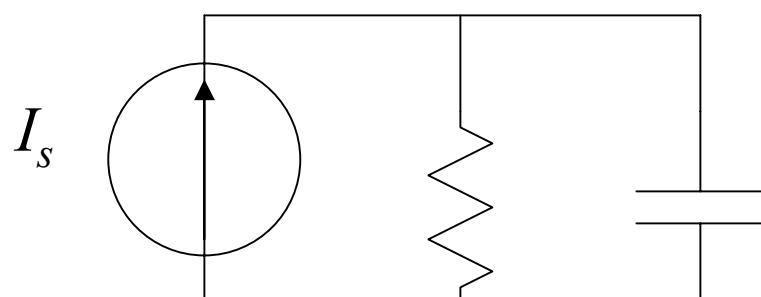


$$v_R = v_c \Rightarrow i_R = \frac{v_c}{R}; \quad i_R + i_c = I_s \Rightarrow RC \frac{dv_c}{dt} + v_c = RI_s$$

$$\Rightarrow v_c(t) = e^{-\frac{t}{RC}} v_c(0) + \frac{1}{RC} \int_0^t e^{-\frac{t-\tau}{RC}} RI_s(\tau) d\tau$$

$$\text{const. } I_s, \quad v_c(t) \rightarrow RI_s (= v_R)$$


Solutions of Simple RL Circuits

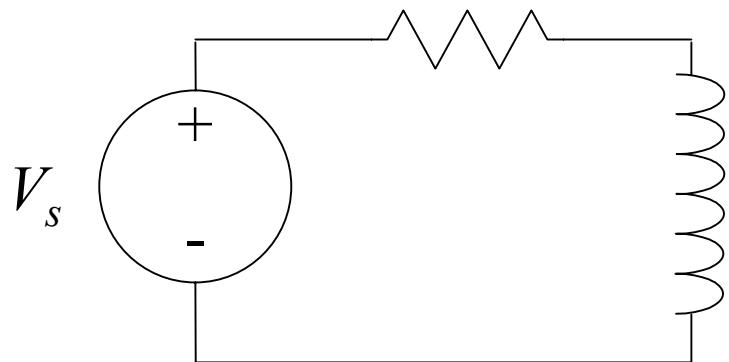

$$V_s = RI_L + L \frac{di_L}{dt} \Rightarrow$$

$$i_L(t) = e^{-\frac{R}{L}t} i_L(0) + \frac{R}{L} \int_0^t e^{-\frac{R}{L}(t-\tau)} \frac{1}{R} V_s(\tau) d\tau$$

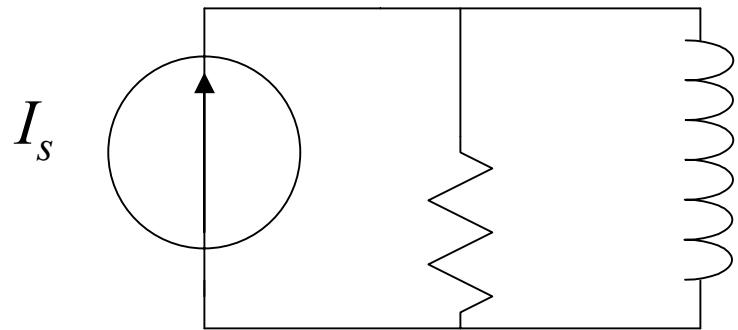
$$\text{const. } V_s, \quad i_L(t) \rightarrow \frac{V_s}{R}$$



$$V_R = V_L \Rightarrow R i_R = L \frac{di_L}{dt}; \quad I_s = i_R + i_L = \frac{L}{R} \frac{di_L}{dt} + i_L$$

$$\Rightarrow i_L(t) = e^{-\frac{R}{L}t} i_L(0) + \frac{R}{L} \int_0^t e^{-\frac{R}{L}(t-\tau)} I_s(\tau) d\tau$$

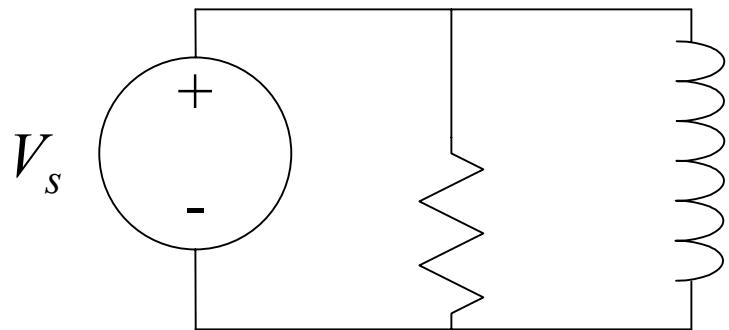
$$\text{const. } I_s, \quad i_L(t) \rightarrow I_s$$



$$v_L = V_s = L \frac{di_L}{dt} \Rightarrow i_L(t) = i_L(0) + \frac{1}{L} \int_0^t V_s(\tau) d\tau$$

$$\text{const. } V_s, \quad i_c(t) = i_c(0) + \frac{V_s}{L} t \rightarrow \infty$$

Solutions of Simple RL Circuits (cont.)

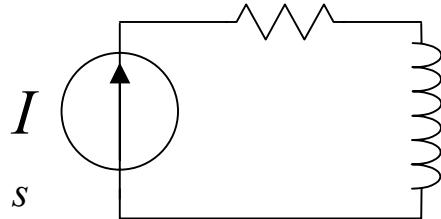

$$i_L = I_s; \quad v_L = L \frac{di_L}{dt} \Rightarrow \\ \text{discont. } I_s, \quad v_L(t) \text{ not well-defined}$$

Solutions of 2nd-Order linear ODEs

Notation

$$\text{ODE: } \frac{d^2y}{dt^2}(t) + a \frac{dy}{dt}(t) + by(t) = x(t) \\ a > 0, \quad b > 0$$

$$\text{char. eqn: } s^2 + as + b = 0$$

$$\text{or } s^2 + 2\zeta\omega_0 s + \omega_0^2 = 0$$

$$\text{or } (s - s_1)(s - s_2) = 0$$

initial conditions:

$$y(0) = y_0, \quad \frac{dy}{dt}(0) = y'_0$$

Solution

$$y(t) = h_1(t)y_0 + h_2(t)y'_0 + \int_0^t g(t-\tau)x(\tau)d\tau$$

Case 1 (simple real roots, $\zeta > 1$):

$$h_1(t) = \frac{s_2}{s_2 - s_1} e^{s_1 t} + \frac{s_1}{s_1 - s_2} e^{s_2 t}; \quad h_2(t) = \frac{-1}{s_2 - s_1} e^{s_1 t} + \frac{-1}{s_1 - s_2} e^{s_2 t}; \\ g(t) = \frac{1}{s_1 - s_2} [e^{s_1 t} - e^{s_2 t}]$$

Case 2 (double real root, $\zeta = 1$):

$$h_1(t) = (1 - s_1 t) e^{s_1 t}; \quad h_2(t) = t e^{s_1 t}; \quad g(t) = t e^{s_1 t}$$

Case 3 (complex roots, $\zeta < 1$):

$$h_1(t) = \left(\cos[\omega_0 \sqrt{1 - \zeta^2} t] + \frac{\zeta}{\sqrt{1 - \zeta^2}} \sin[\omega_0 \sqrt{1 - \zeta^2} t] \right) e^{-\zeta \omega_0 t}; \\ h_2(t) = g(t) = \frac{\sin[\omega_0 \sqrt{1 - \zeta^2} t]}{\omega_0 \sqrt{1 - \zeta^2}} e^{-\zeta \omega_0 t}$$