

EEE 202: TEST 3

NAME: _____ SOLUTIONS _____

3 Problems, equal credit, 75', Closed Book&Notes, 1 sheet of formulae allowed


Problem 1.

The current across a $1\mu\text{F}$ capacitor is shown in the following figure. The capacitor starts at $t = 0$ completely discharged. Plot the capacitor voltage. Find the energy stored in the capacitor at $t = 10$ ms.

We use $v(t) = \frac{1}{C} \int i(t) dt$

At 1ms, the voltage is
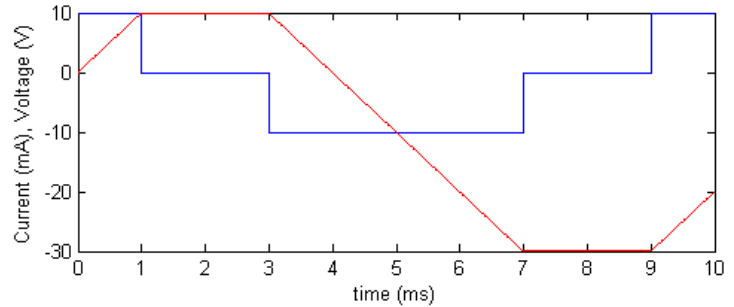
$$v(t) = \frac{1}{1e-6} 1e - 3 \times 10e - 3 = 10(V)$$



Similarly, the ending voltage is $v(10\text{ms}) = -20(V)$

The capacitor energy at that time is $E(10\text{ms}) = \frac{1}{2} C v^2(10\text{ms}) = 0.2\text{mJ}$


Problem 2. In the following circuit, find the voltage V_o for $t > 0$. (The switch closes at $t = 0$.)

1. IC: $V_o(0^-) = V_o(0^+) = 0$.

2. FV: $V_o(\infty) = \frac{2k}{1k+2k} 5 = \frac{10}{3} (V)$.

3. TC: $R_{TH} = 3k + 1k || 2k = \frac{11}{3} k(\Omega)$
 $\Rightarrow \tau = R_{TH} C = 0.367(s)$.

Solution: $V_o(t) = FV + (IC - FV)e^{-t/\tau} = \frac{10}{3} (1 - e^{-\frac{t}{0.367}}) (V)$

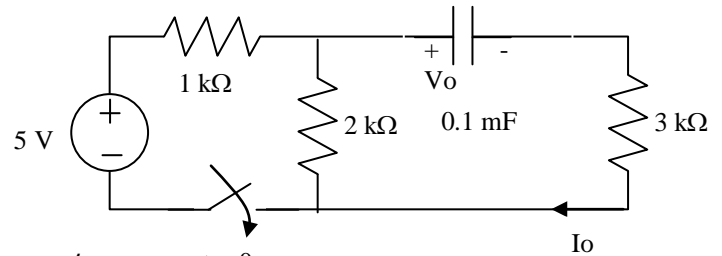

Problem 3. In the following circuit, find the current I_o for $t > 0$. (The switch opens at $t = 0$.)

1. IC: $V_o(0^-) = V_o(0^+) = \frac{2k}{1k+2k} 5 = \frac{10}{3} (V)$.

1. IC: $I_o(0^+) = -\frac{V_o(0^+)}{2k+3k} = -\frac{2}{3} m(A)$.

2. FV: $I_o(\infty) = 0$.

3. TC: $R_{TH} = 3k + 3k = 5k(\Omega)$
 $\Rightarrow \tau = R_{TH} C = 0.5(s)$.

Solution: $I_o(t) = FV + (IC - FV)e^{-t/\tau} = -\frac{2}{3} e^{-\frac{t}{0.5}} m(A)$

